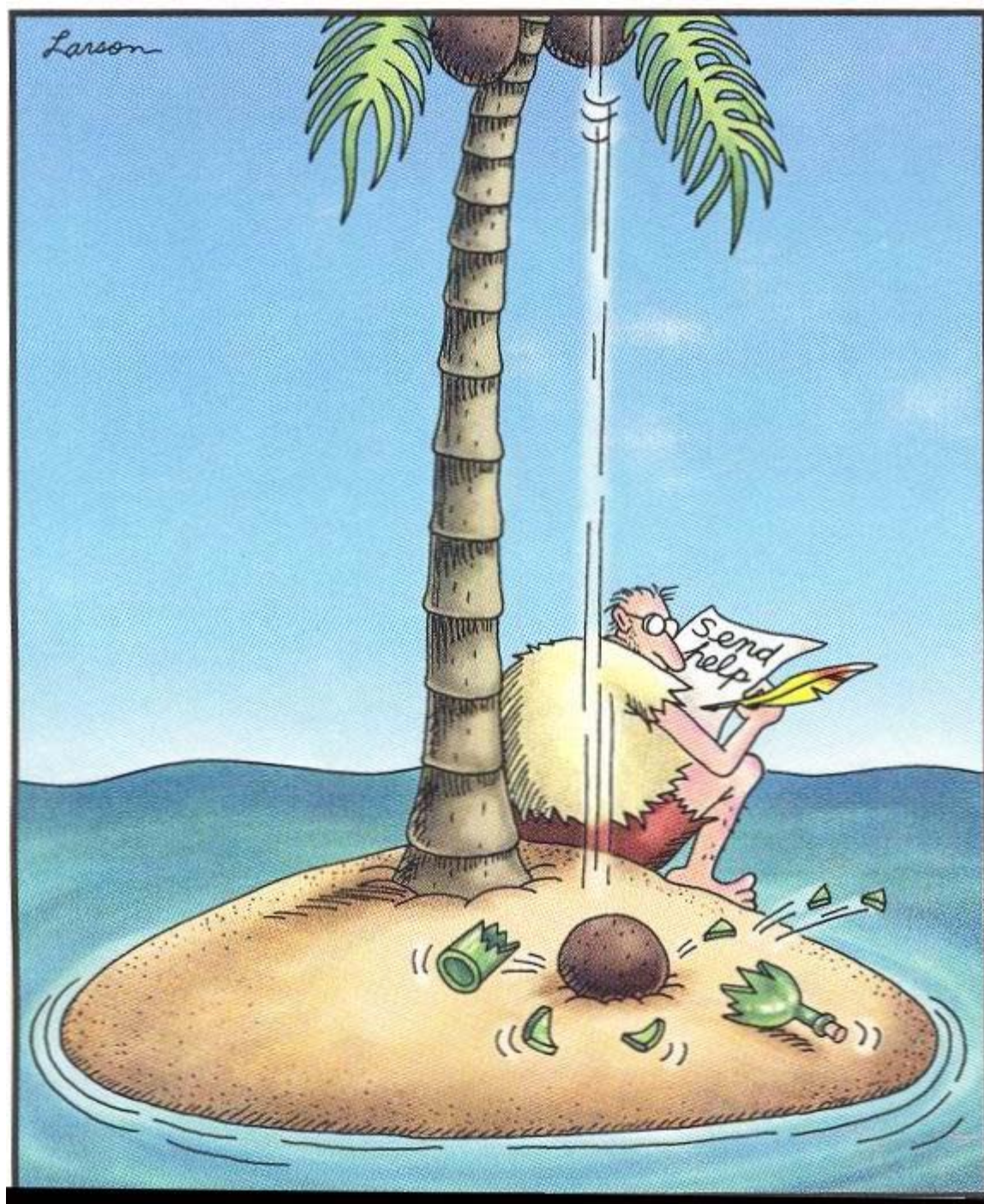


# AC Circuits



# Review

- Magnetic flux  $\Phi_B = \int \vec{B} \cdot d\vec{A}$


- **Faraday's law** (one loop) for emf ( $\mathcal{E}$ ) (induced voltage)

$$\mathcal{E} = -\frac{d\Phi_B}{dt}$$

- Faraday's law (N loops)

$$\mathcal{E} = -N \frac{d\Phi_B}{dt}$$

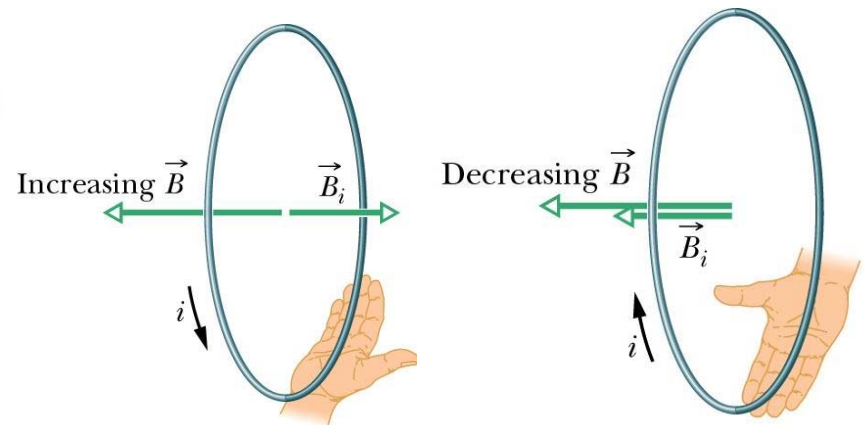- **Lenz's law** – induced emf gives rise to a current whose  $B$  field opposes the change in flux that produced it



# Review for Inductor


- **Inductor** is a device used to produce and store a desired  $B$  field (e.g. solenoid)
- A current  $i$  in an inductor with  $N$  turns produces a magnetic flux,  $\Phi_B$ , in its central region
- **Inductance,  $L$**  is defined as
- Inductance per unit length of a **solenoid**
  - Depends only on geometry of device (like capacitor)

$$L = \frac{N\Phi_B}{i}$$

$$\frac{L}{l} = \mu_0 n^2 A$$
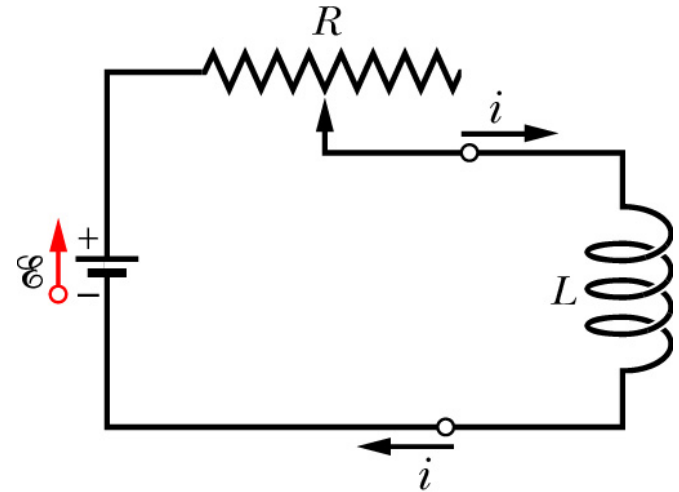
# Inductor in a circuit

- A changing current in a coil generates a self-induced emf,  $\mathcal{E}_L$  in the coil
- Process is called self-induction
- Change current in coil using a variable resistor,  $\mathcal{E}_L$  will appear in coil only while the current is changing



$$L = \frac{N\Phi_B}{i}$$

$$\mathcal{E}_L = -N \frac{d\Phi_B}{dt} = -\frac{d(N\Phi_B)}{dt} = -\frac{d(Li)}{dt} = -L \frac{di}{dt}$$

# EMF of an Inductor

- Induced emf only depends on rate of change of current, not its magnitude
- Direction of  $\mathcal{E}_L$  follows Lenz's law and opposes the change in current
- Self-induced  $V_L$  across inductor



- Ideal inductor

$$V_L = \mathcal{E}_L$$

- Real inductor (like real battery) has some internal resistance

$$V_L = \mathcal{E}_L - iR$$

$$\mathcal{E}_L = -L \frac{di}{dt}$$

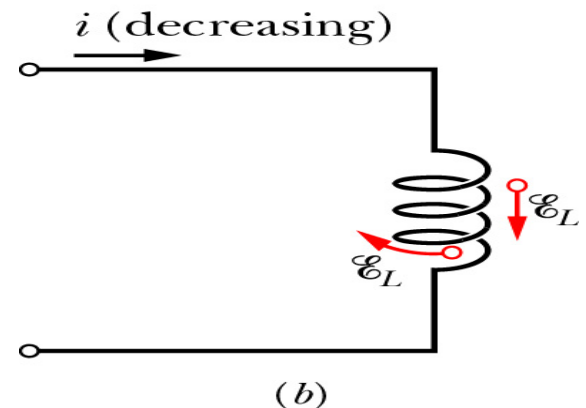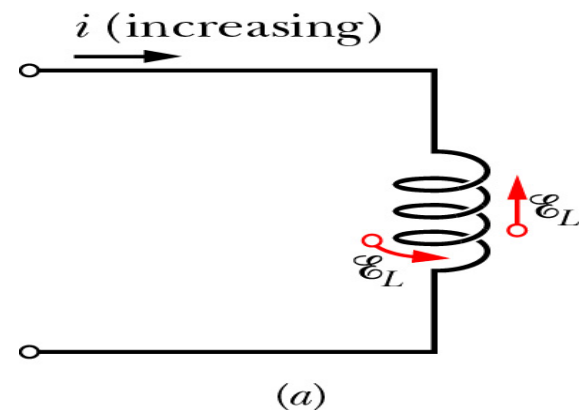


# RL circuit

- **RL circuit** is a resistor and inductor in series
- Close switch to point a
  - **Initially**  $i$  is increasing through inductor so  $\mathcal{E}_L$  opposes rise and  $i$  through  $R$  will be


$$i < \mathcal{E}/R$$

- **Long time later**,  $i$  is constant so  $\mathcal{E}_L=0$  and  $i$  in circuit is

$$i = \mathcal{E}/R$$

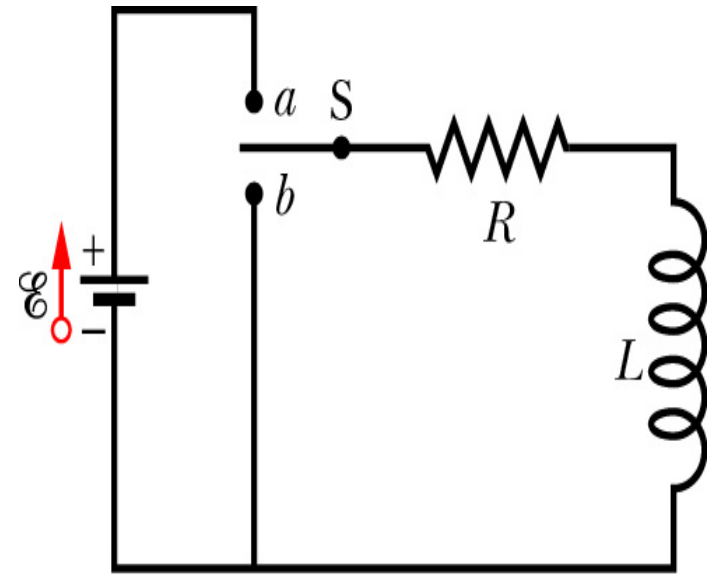



$$\mathcal{E}_L = -L \frac{di}{dt}$$

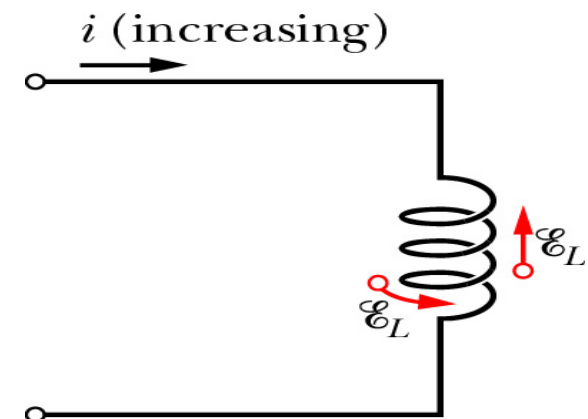
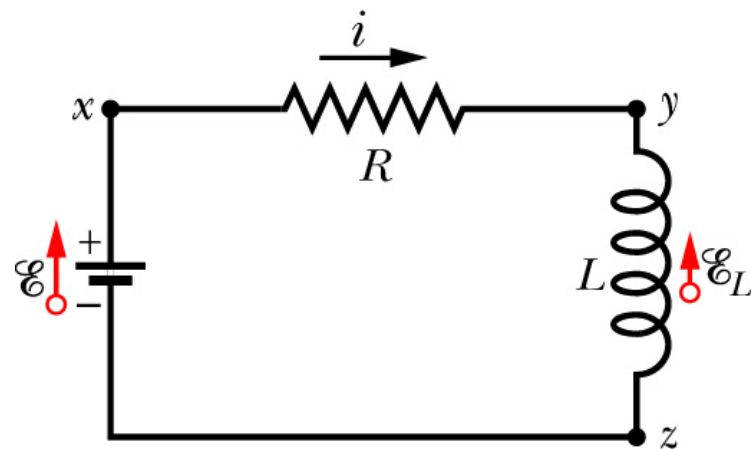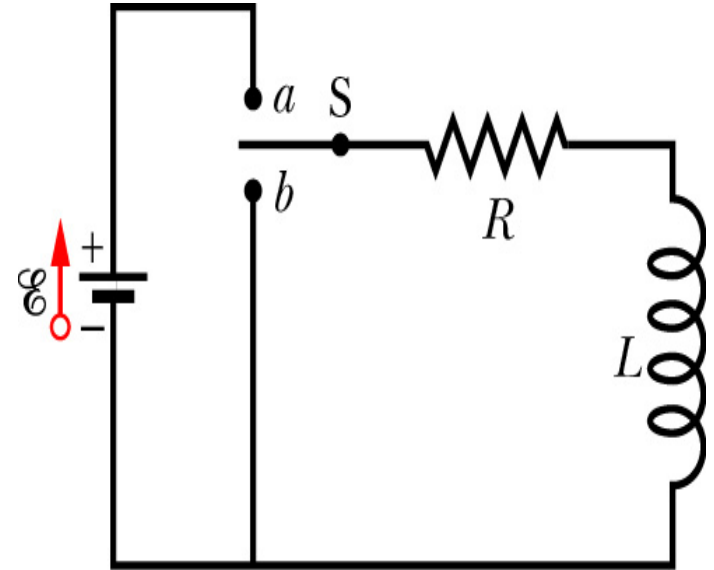
# RL circuit

- Initially an inductor acts to oppose changes in current through it
- Long time later inductor acts like ordinary conducting wire
- Apply loop rule right after switch has been closed at a

$$\mathcal{E} - iR - L \frac{di}{dt} = 0$$



# Solution RL circuit equation


- Assume  $i = Ae^{\alpha t} + B$  and replace in  $\mathcal{E} - iR - L\frac{di}{dt} = 0$

  $-RAe^{\alpha t} - BR - L\alpha Ae^{\alpha t} = 0$  (a)

- But boundary conditions:

- At  $t=0$ ,  $i = 0$

- At  $t=\infty$ ,  $i = \mathcal{E}/R$

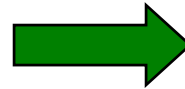

$$A = -B$$

$$\alpha < 0; \quad B = \mathcal{E}/R$$

(b)

- Solving (a) and (b):

$$i = \frac{\mathcal{E}}{R} \left( 1 - e^{-t/\tau_L} \right)$$

$$\tau_L = \frac{L}{R}$$



# Solving RL circuit equation

- Differential equation similar to capacitors


$$\mathcal{E} = iR + L \frac{di}{dt}$$

- Solution is

$$i = \frac{\mathcal{E}}{R} \left( 1 - e^{-t/\tau_L} \right)$$

- Inductive time constant is

$$\tau_L = \frac{L}{R}$$

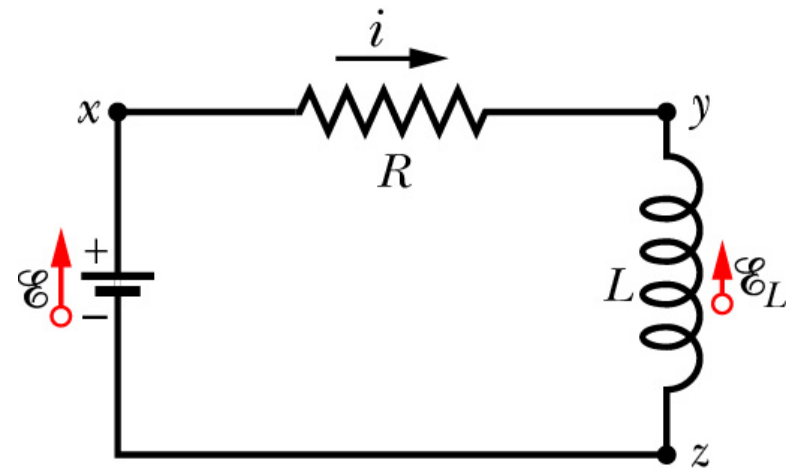

- Satisfies conditions:

- At  $t=0$ ,  $i = 0$
- At  $t=\infty$ ,  $i = \mathcal{E}/R$



# Charging and discharging RL circuit

- Now move switch to position b so battery is out of system
- Current will decrease with time and loop rule gives

$$iR + L \frac{di}{dt} = 0$$

- Solution is
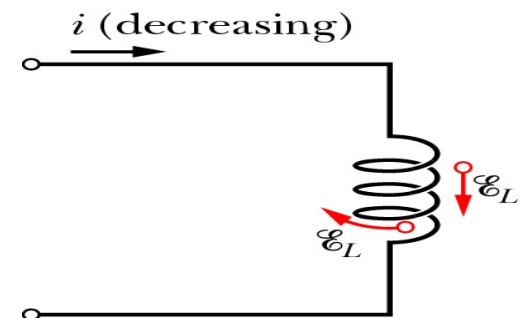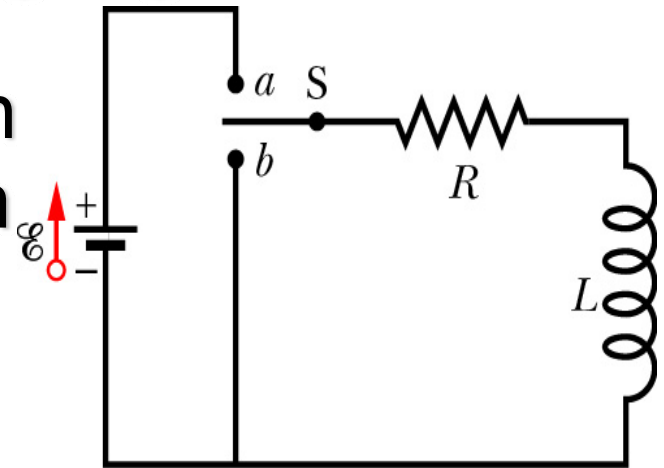
$$i = \frac{\varepsilon}{R} e^{-t/\tau_L} = i_0 e^{-t/\tau_L}$$



- Satisfies conditions
  - At  $t=0$ ,  $i = i_0 = \varepsilon/R$
  - At  $t=\infty$ ,  $i = 0$

# RL circuits Summary

- Circuit is closed (switch to "a")


$$i = \frac{E}{R} \left(1 - e^{-t/\tau_L}\right)$$

- Circuit is opened (switch to "b")

$$i = \frac{E}{R} e^{-t/\tau_L} = i_0 e^{-t/\tau_L}$$

- Time constant is

$$\tau_L = \frac{L}{R}$$


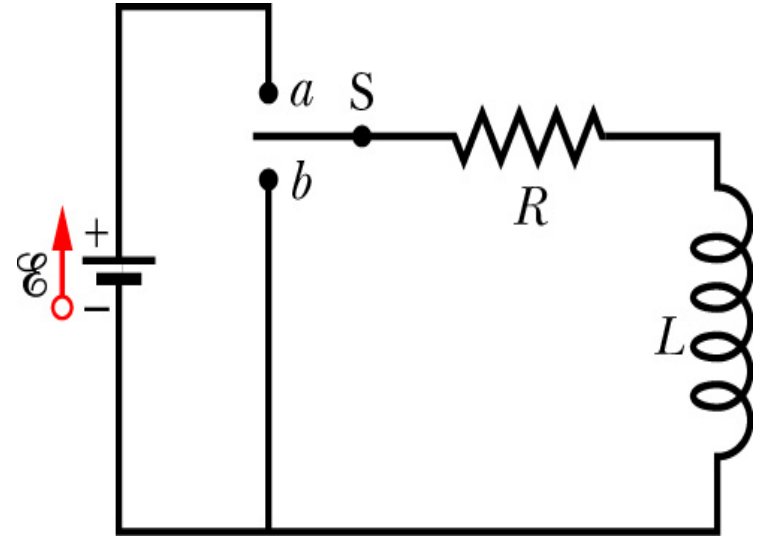


Switch at a, current through inductor is:

- Initially  $i = 0$  (acts like **broken wire**)
- Long time later  $i = \mathcal{E}/R$  (acts like **simple wire**)
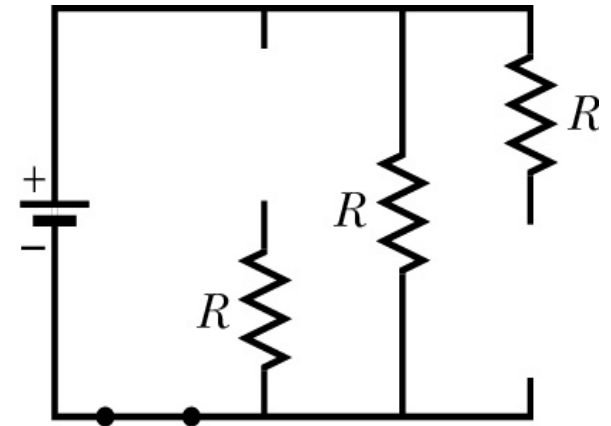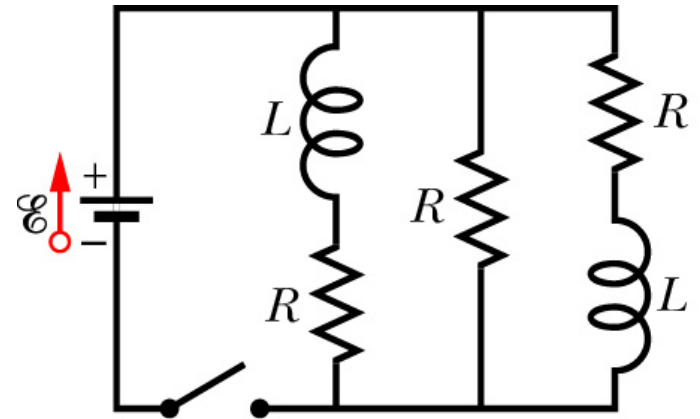
# Exercise

- Have a circuit with resistors and inductors
- What is the current through the battery **just after** closing the switch?
- Inductor oppose change in current through it
- Right after switch is closed, current through inductor is 0
- **Inductor acts like broken wire**





# Exercise

- Apply loop rule

$$\mathcal{E} - iR = 0$$

- Immediately after switch closed, current through the battery is

$$i = \frac{\mathcal{E}}{R}$$

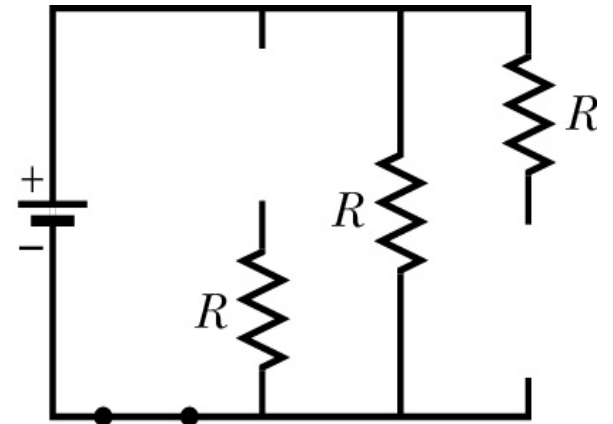
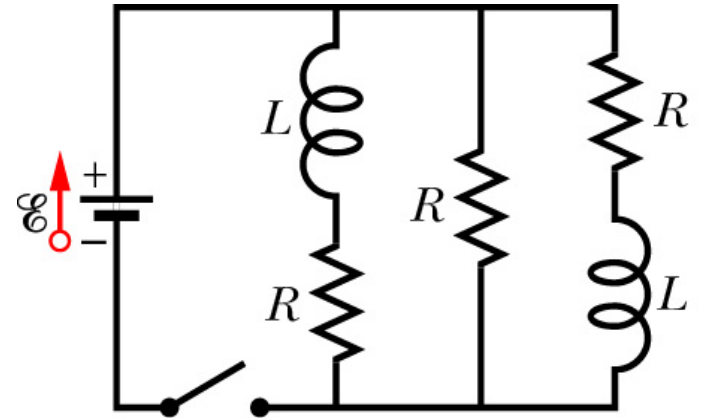


# Exercise

- What is the current through the battery a **long time after** the switch has been closed?
- Currents in circuit have reached equilibrium so **inductor acts like simple wire**
- Circuit is 3 resistors in parallel

$$i = \frac{E}{R_{eq}}$$

$$R_{eq} = \frac{R}{3}$$

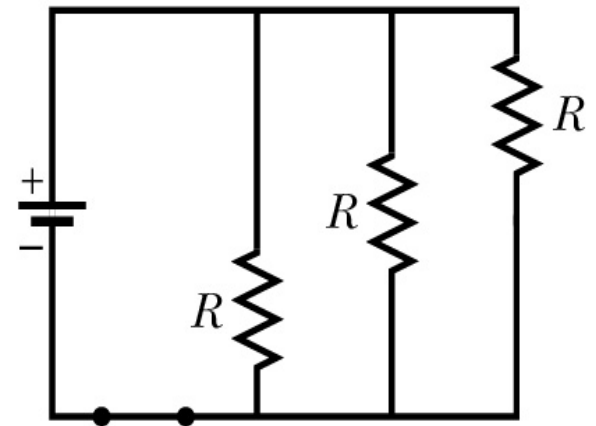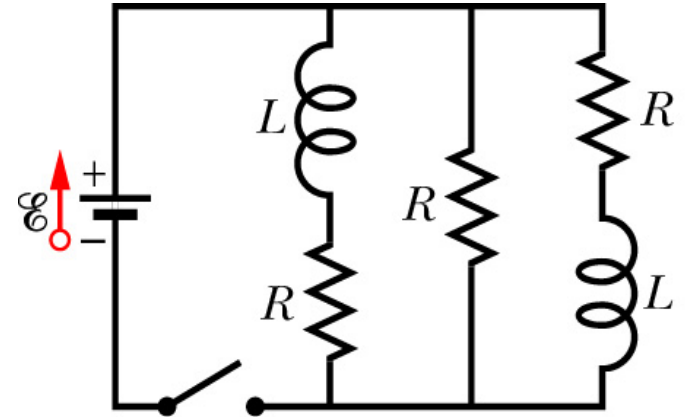

(c)


# Energy stored in an inductor

- How much energy is stored in a  $B$  field?
- Conservation of energy expressed in loop rule

$$\mathcal{E} = L \frac{di}{dt} + iR$$

- Multiply each side by  $i$
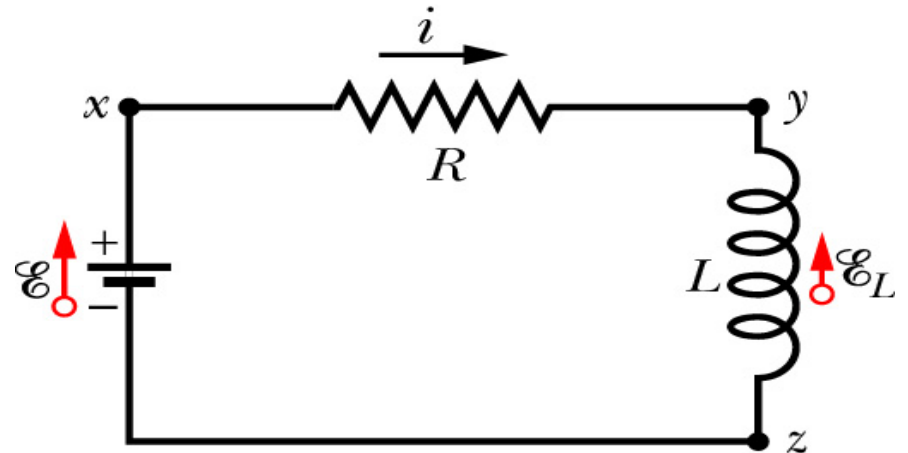
$$\mathcal{E}i = Li \frac{di}{dt} + i^2 R$$



- $P=i\mathcal{E}$  is the rate at which the battery delivers energy to rest of circuit
- $P=i^2 R$  is the rate at which energy appears as thermal energy in resistor

# Energy stored in an inductor

- Middle term is rate at which energy  $dU_B/dt$  is stored in the  $B$  field

$$\frac{dU_B}{dt} = Li \frac{di}{dt}$$

- Energy stored in magnetic field

$$U_B = \frac{1}{2} Li^2$$

- Similar to energy stored in electric field

$$U_E = \frac{1}{2} \frac{q^2}{C}$$