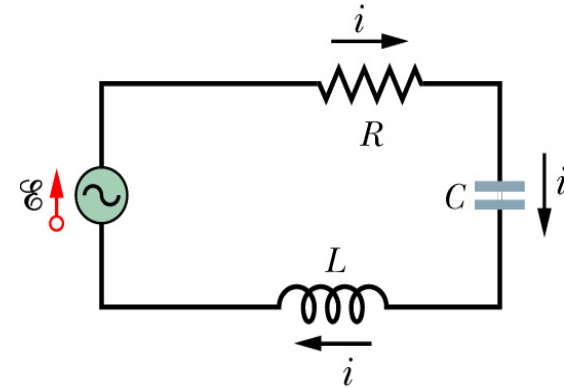


RLC circuits

- End result:

$$I = \frac{\mathcal{E}_m}{\sqrt{R^2 + \left(\omega_d L - \frac{1}{\omega_d C} \right)^2}}$$



- I is largest when bottom is small


$$\omega_d L = \frac{1}{\omega_d C}$$

- Or

$$\omega_d = \sqrt{\frac{1}{LC}} = \omega$$

ω is also called the resonance frequency (in the homework)

$$\omega = \omega_R = 2\pi f_R$$

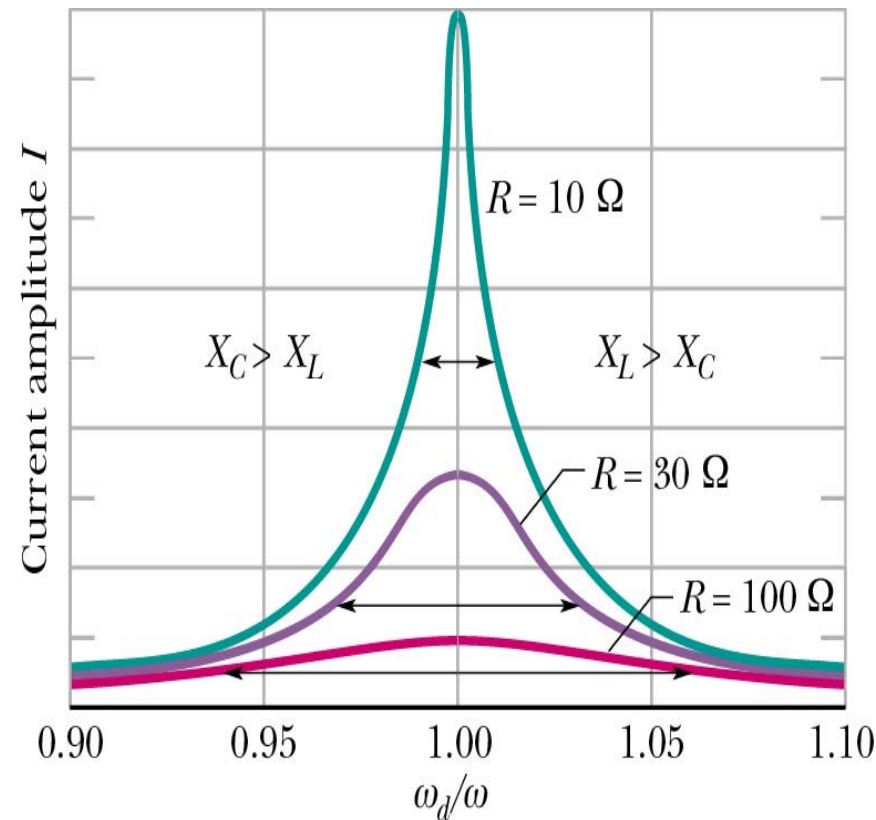


AC circuits

- RLC circuit – resistor, capacitor and inductor in series
- Apply alternating emf

$$\mathbf{E} = \mathbf{E}_m \sin \omega_d t$$

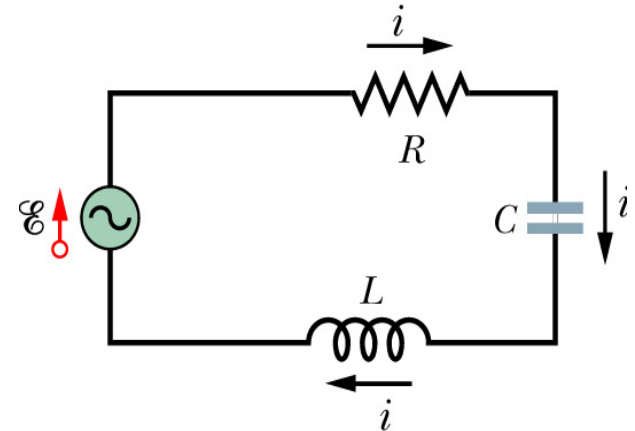- Elements are in series so same current is driven through each
- From the loop rule, at any time t , the sum of the voltages across the elements must equal the applied emf



$$i = I \sin(\omega_d t - \phi)$$

$$\mathbf{E} = v_R + v_C + v_L$$

AC circuits

$$I = \frac{E_m}{\sqrt{R^2 + (X_L - X_C)^2}} = \frac{E_m}{Z}$$

$$\tan \phi = \frac{X_L - X_C}{R}$$

- Define **impedance, Z** to be

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

- Using reactances
rewrite current as

$$X_L = \omega_d L$$

$$X_C = \frac{1}{\omega_d C}$$

$$I = \frac{E_m}{\sqrt{R^2 + \left(\omega_d L - \frac{1}{\omega_d C} \right)^2}}$$

AC circuits

- Relationship between reactances and frequencies

- From $X_L = \omega_d L$ $X_C = \frac{1}{\omega_d C}$

- We have $\frac{X_L}{X_C} = (\omega_d)^2 LC$

- or $\frac{X_L}{X_C} = \frac{(\omega_d)^2}{\omega^2}$

AC circuits

- Instantaneous rate which energy is dissipated (power) in a resistor is



$$P = i^2 R$$

- But $i = I \sin(\omega_d t - \phi)$


$$P = I^2 R \sin^2(\omega_d t - \phi)$$

- Want average (rms) rate
 - Average over complete cycle T

$$\langle \sin^2 \theta \rangle = 1/2$$

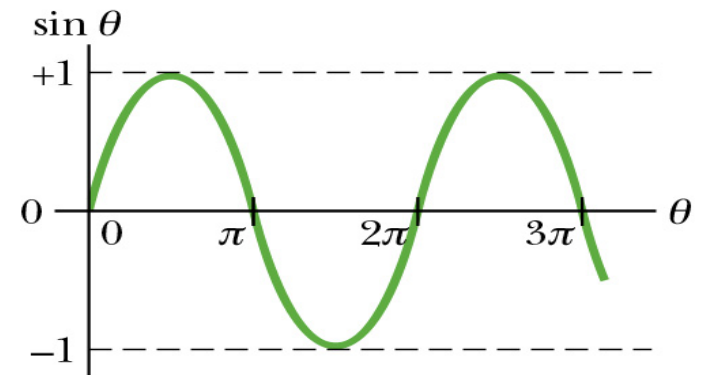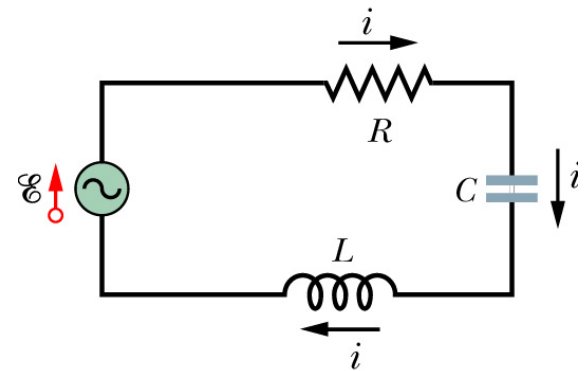

(a)

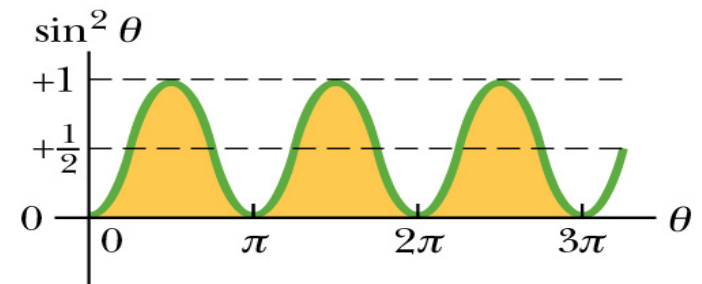

...

AC circuits

- For alternating current circuits define **root-mean-square or rms** values for i , V and emf

$$I_{rms} = \frac{I}{\sqrt{2}} \quad V_{rms} = \frac{V}{\sqrt{2}} \quad E_{rms} = \frac{E}{\sqrt{2}}$$

- Ammeters, voltmeters - give rms values
- The average (rms) power dissipated by resistor in an ac circuit is

$$P_{rms} = \frac{I^2 R}{2} = \left(\frac{I}{\sqrt{2}} \right)^2 R$$

$$P_{rms} = I_{rms}^2 R$$

EM Oscillations

- Write average power in another form using

$$I_{rms} = \frac{E_{rms}}{Z}$$


$$P_{avg} = I_{rms}^2 R = \frac{E_{rms}}{Z} I_{rms} R = E_{rms} I_{rms} \frac{R}{Z}$$

- Using phasor and amplitude relations

$$\cos \phi = \frac{V_R}{E_m} = \frac{IR}{IZ} = \frac{R}{Z}$$

- Rewrite average power as

$$P_{avg} = E_{rms} I_{rms} \cos \phi$$

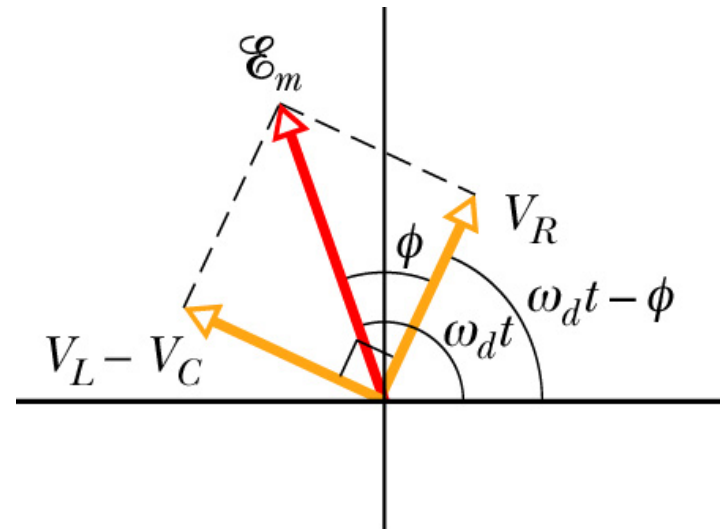

AC circuits

- If ac circuit has only resistive load $Z=R$ (e.g. at the resonance frequency)

$$P_{rms} = E_{rms} I_{rms}$$

- Trade-off between current and voltage
 - For general use want low voltage
 - Means high current but

$$P_{rms} = I_{rms}^2 R$$

- General energy transmission rule:
Transmit at the highest possible voltage and the lowest possible current