

Ohm's Law

- So far have assumed that R is independent of the magnitude and polarity of the applied V

$$R = \frac{V}{i}$$


- This is known as **Ohm's law**

$$V = iR$$

- Ohm's law is not generally valid, but it is a good empirical rule for most systems

Ohm's Law

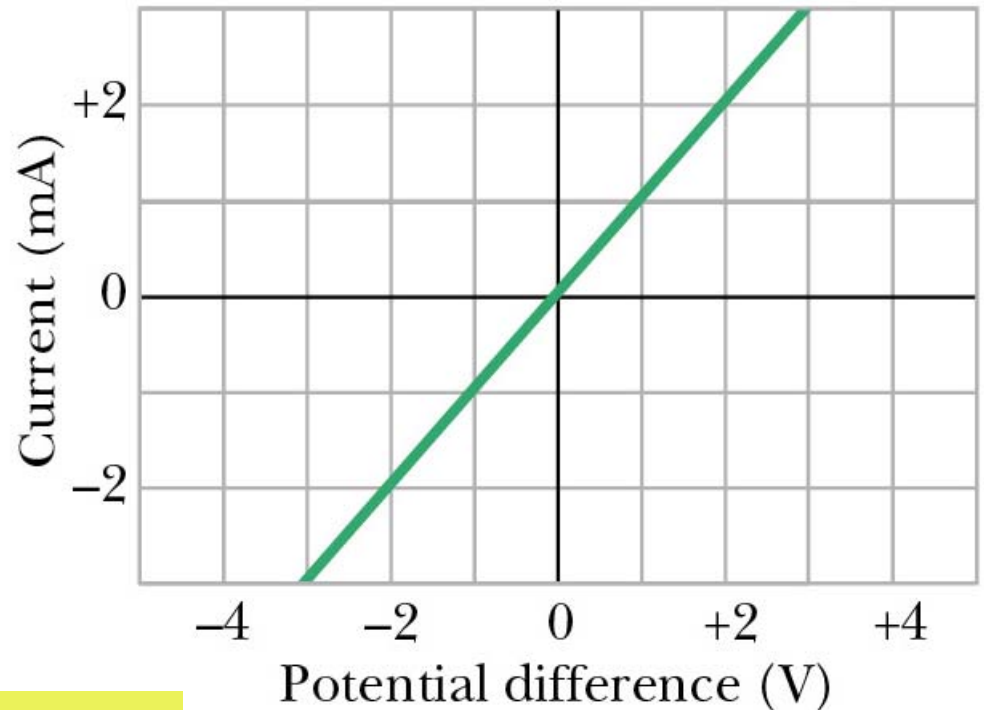- **Ohm's law** asserts that current through a device is always directly proportional to the V applied to the device
- Plot of i vs. V is a straight line
 - Slope (i/V) is the same for all values of V




$$R = V/i$$

- A conducting device obeys Ohm's law when R is independent of size and direction of V


Semiconductors

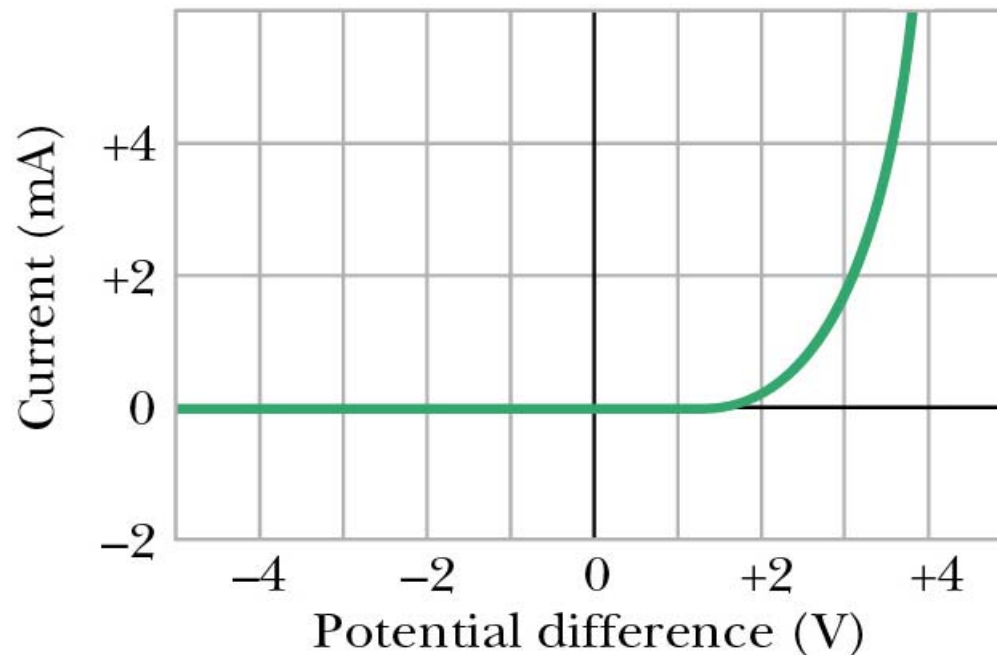- What about this graph?
- It's for a semiconductor
 - (Not all materials obey Ohm's law)



Superconductors

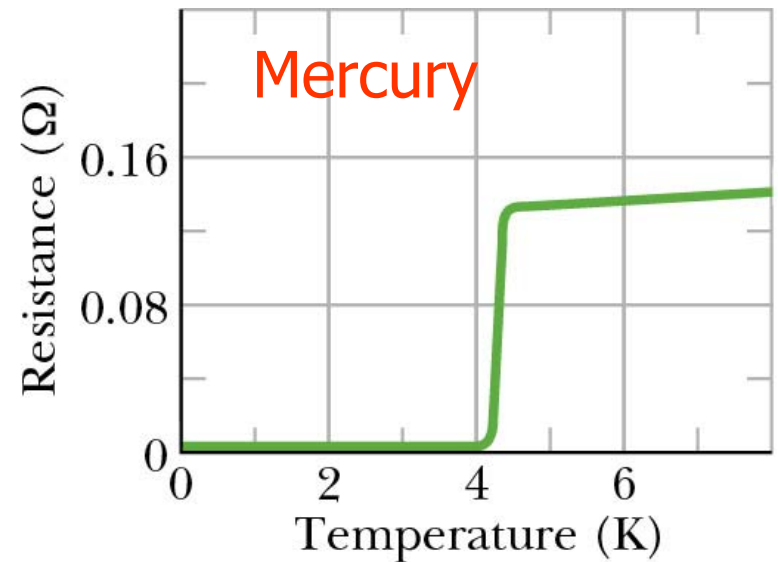- Superconductors: R goes to zero at some finite T
- Once charges start moving no thermal losses - current forever
- Temperatures are usually very low (4-20 K)




Electric Power

- Calculate the amount of power, P , in a circuit

$$P = \frac{dU}{dt}$$

$$dU = dq V = i dt V$$

$$P = iV$$

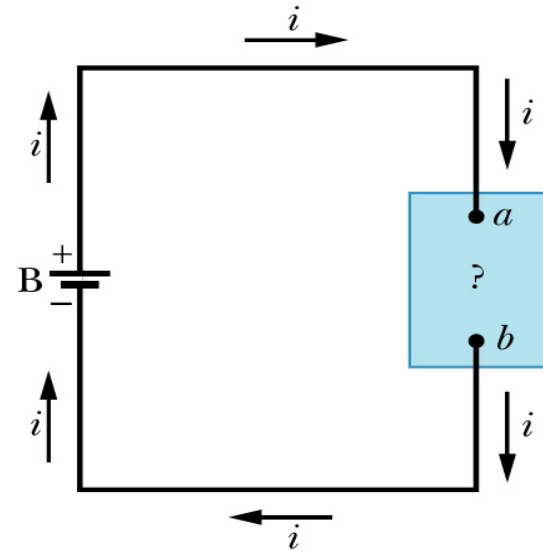

- SI unit is watt, W

$$1W = 1V \cdot A$$

Electric Power

- Transfer potential energy, U , to some other form

$$P = iV$$

- For resistors energy is transferred to thermal energy – heat


$$R = \frac{V}{i}$$



- Use resistance definition to find

$$P = i^2 R$$


$$P = \frac{V^2}{R}$$

Electromotive Force

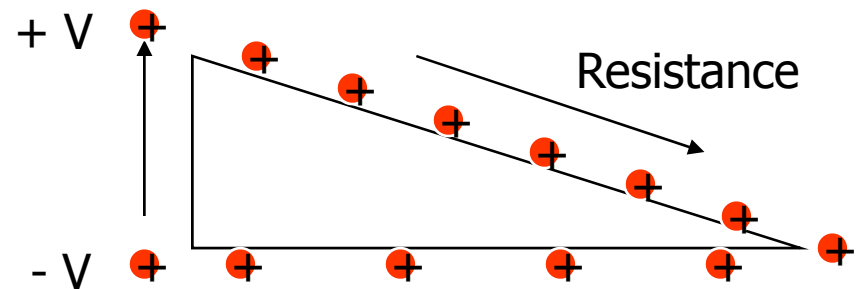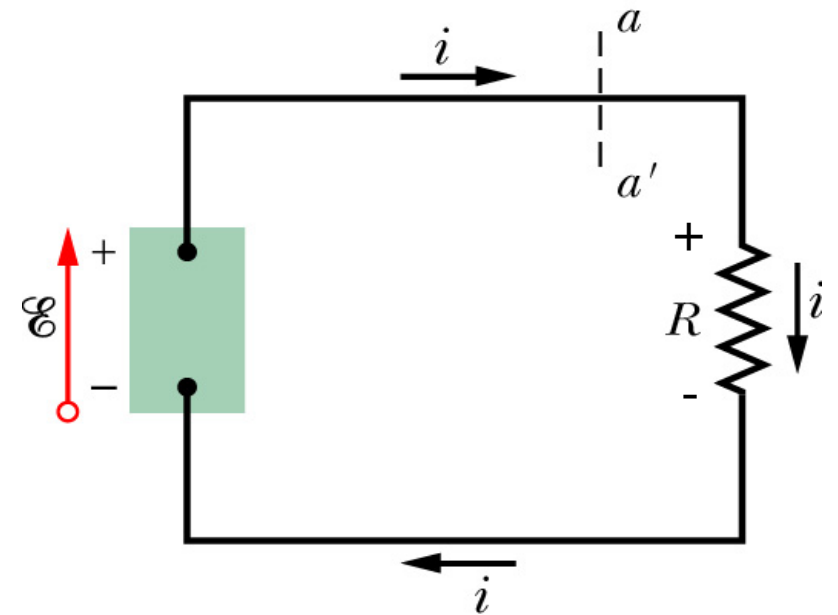- **emf device** (label terminal at higher V as $+$ and lower V as $-$)
- Draw emf, , arrow from $-$ to $+$ terminal
- Label the R with a $+$ and $-$
- $+$ charge carriers are moved against the *Electric* field in emf device from lower ($-$) to higher ($+$) V . The emf must do work on the charge. Normally this is supplied by chemical energy.



Electromotive Force

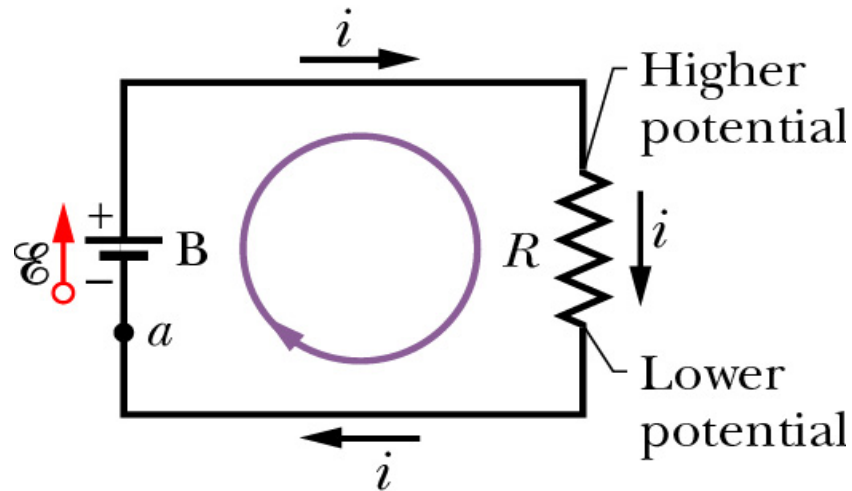


Ohm's Law:

$$\mathbf{E = iR}$$

(the E supplies the potential difference V)


Simplest Circuit

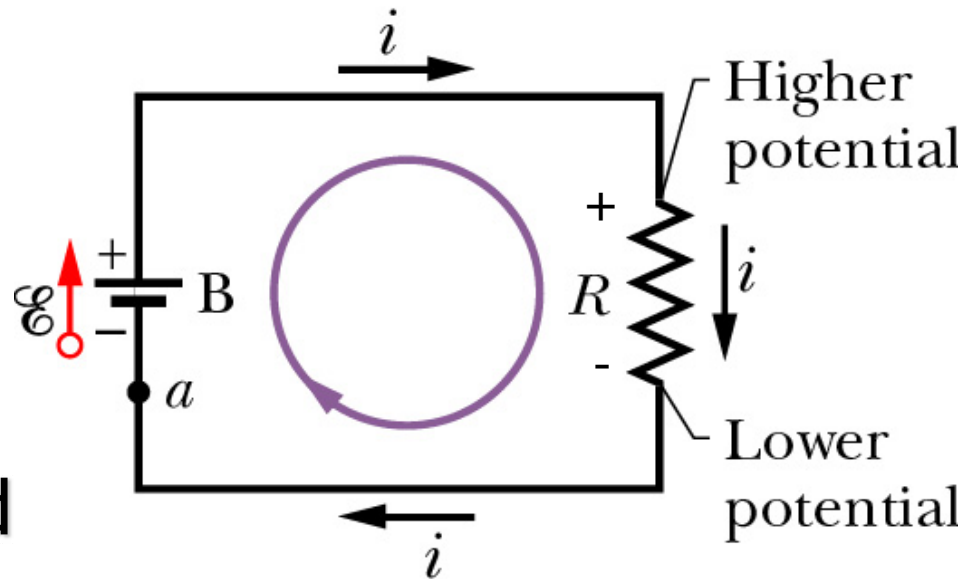- Calculate the current in single-loop circuit
- Use potential method (as called by the text book).
- Travel around circuit in either direction and algebraically add potential differences



Simplest Circuit

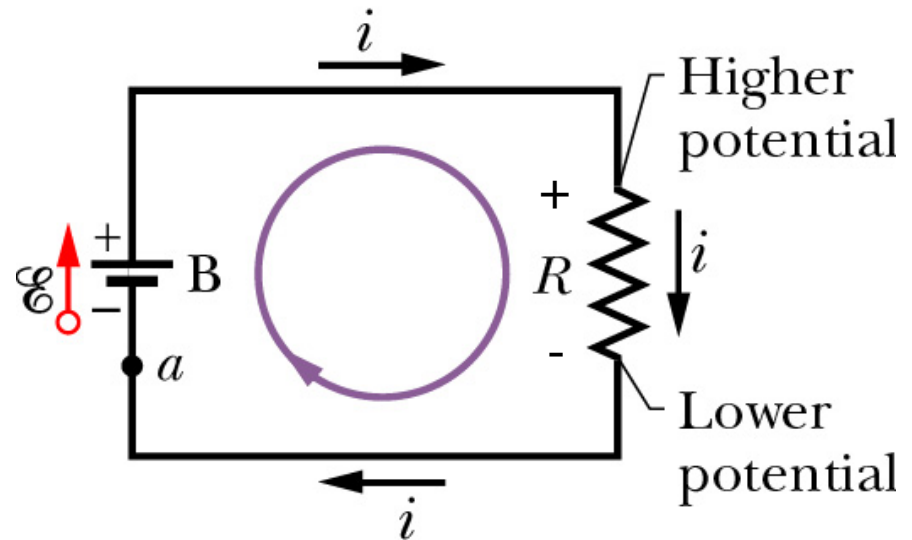- Start at point a with potential V_a
- Move clockwise around circuit
- Pass through battery moving to higher V , change in V is $+E$
- Neglect resistance of connecting wires




$$V_a + E$$

Simplest Circuit

- Top of resistor at same V as battery
- Pass through resistor V decreases and

$$V = iR$$

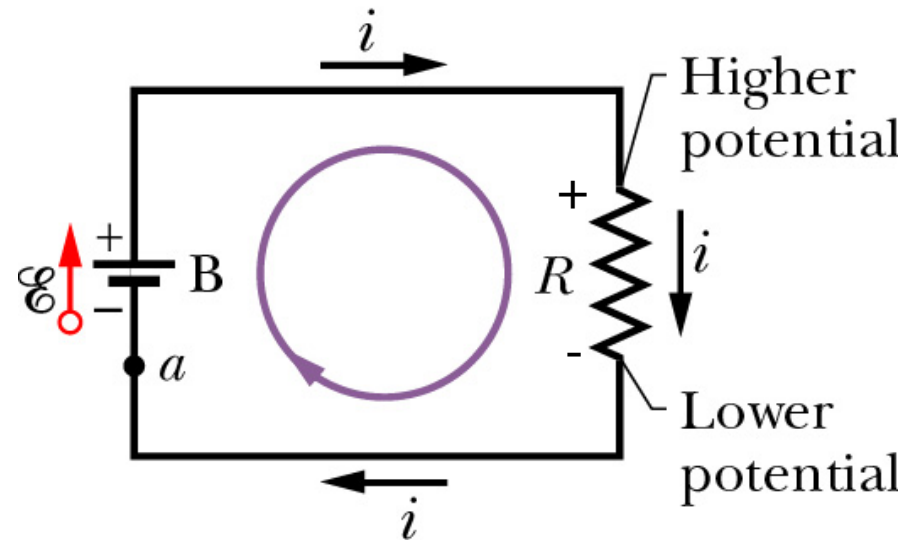- Return to point a on bottom wire back to potential V_a so




$$V_a + \mathcal{E} - iR = V_a$$

Simplest Circuit

- We get back to Ohm's Law

$$\mathbf{E = iR}$$

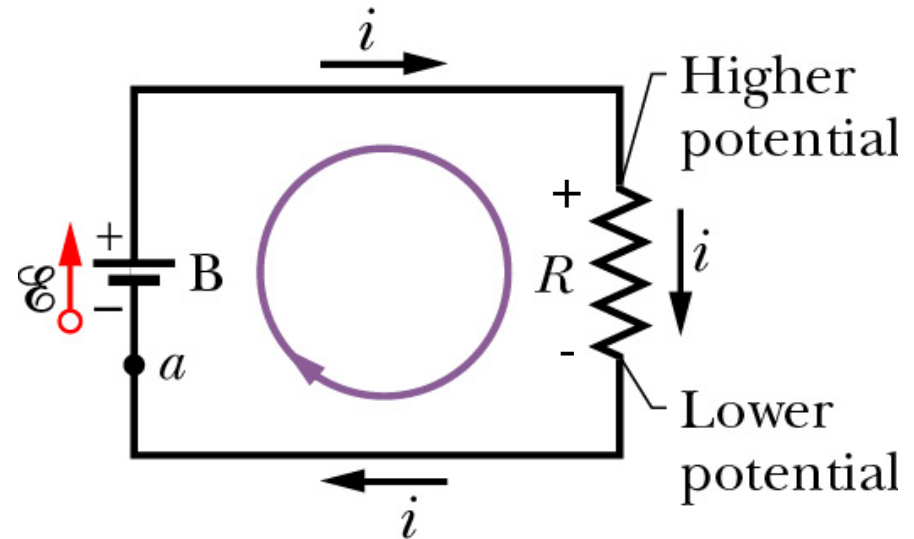

- Could move around circuit counterclockwise

$$V_a - \mathbf{E} + iR = V_a$$


$$\mathbf{E = iR}$$

Kirchoff's rules

- **Kirchoff's loop rule** – in traversing a circuit loop the sum of the changes in V is zero, $\Delta V = 0$

How do we add the changes in V ?

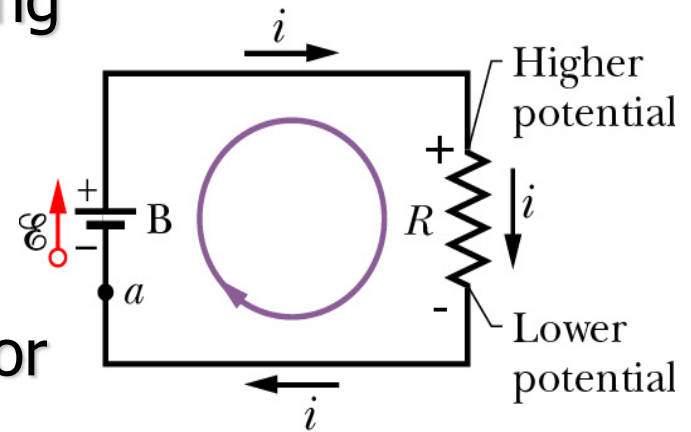- **Resistance** – Move through resistor in direction of current $V = -iR$ (- because it is down the hill), in opposite direction $V = +iR$ (+ because we move up the hill)
- **Emf** – Move lower (-) to (+) adds potential and $V = +E$, in the opposite direction $V = -E$.




Exercise

- A) What direction should the emf arrow point?

RIGHTWARD

- B) Rank magnitude of current at points a, b, and c.

All same

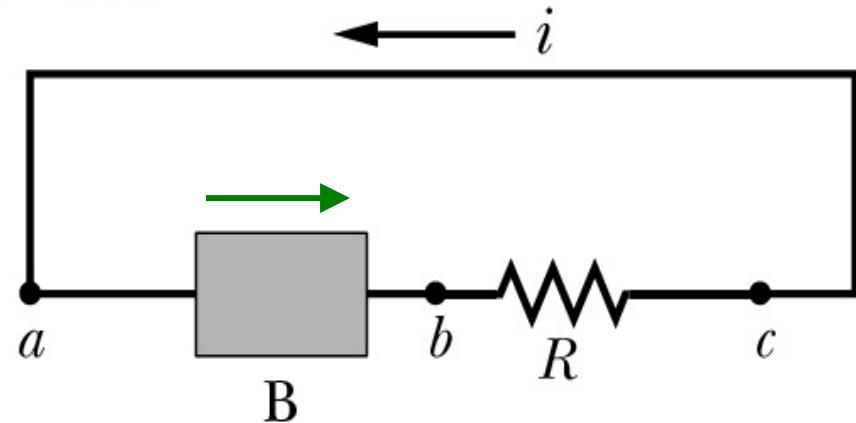


- C) Rank V and U.

b, then a and c tie

Batteries

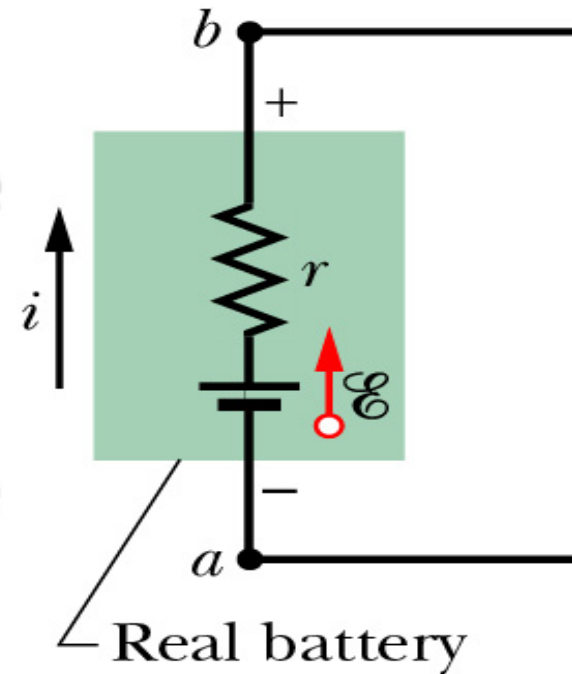- So far assumed **ideal battery** – has no internal resistance
- **Real battery** has internal resistance to movement of charge
- Not in circuit $V = E$ of battery
- If current present $V = E - iR$, where R is the internal resistance of the battery



Circuits with batteries


- Put **real** battery in circuit
- Using Kirchhoff's loop rule and starting at point a gives

$$E - ir - iR = 0$$

$$E = i(r + R)$$

- For ideal battery, $r = 0$ and we get same as before



$$E = iR$$

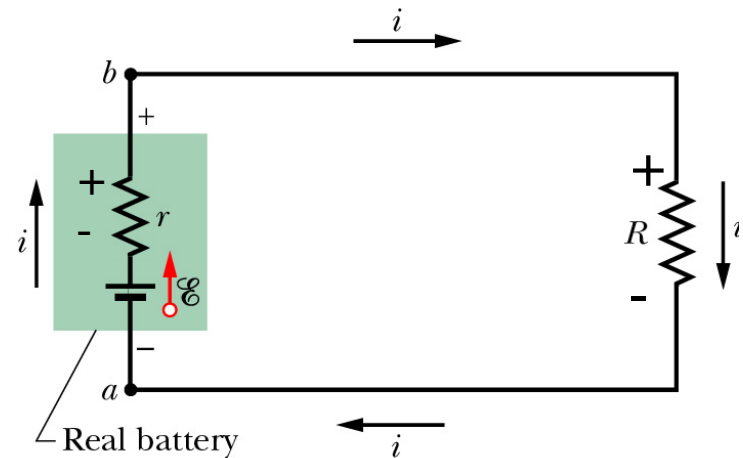

Potential gains and drops

- Can represent changes in potential graphically


$$\mathcal{E} - ir - iR = 0$$

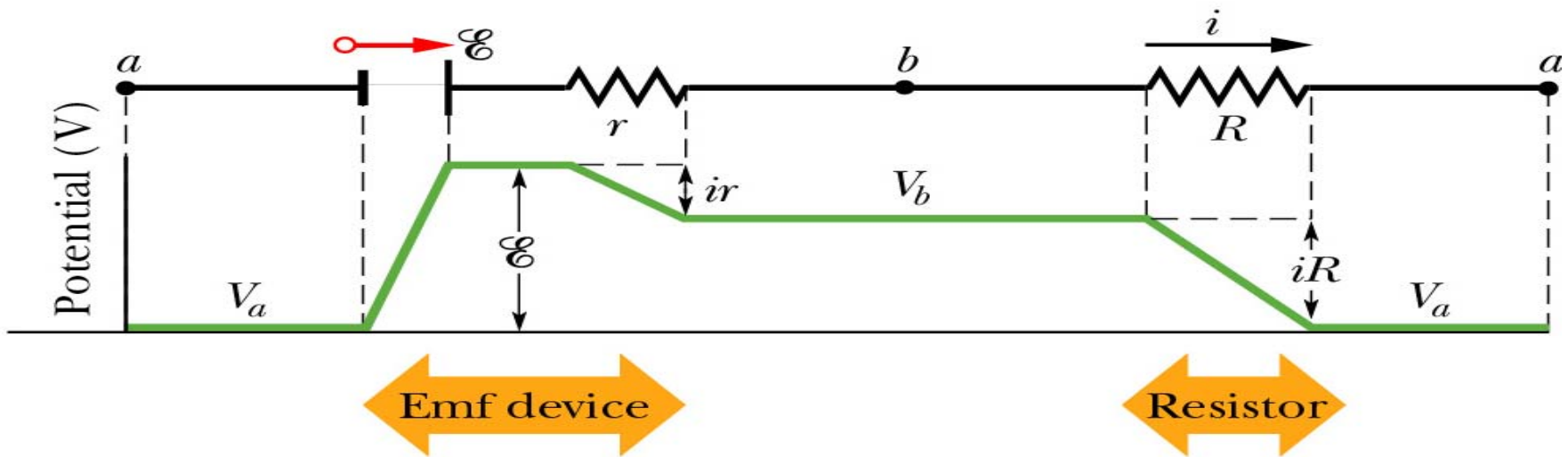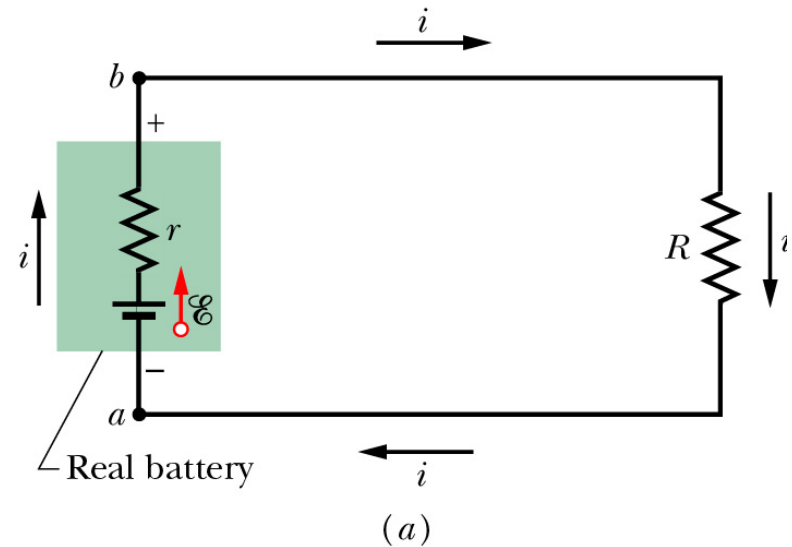

(b)

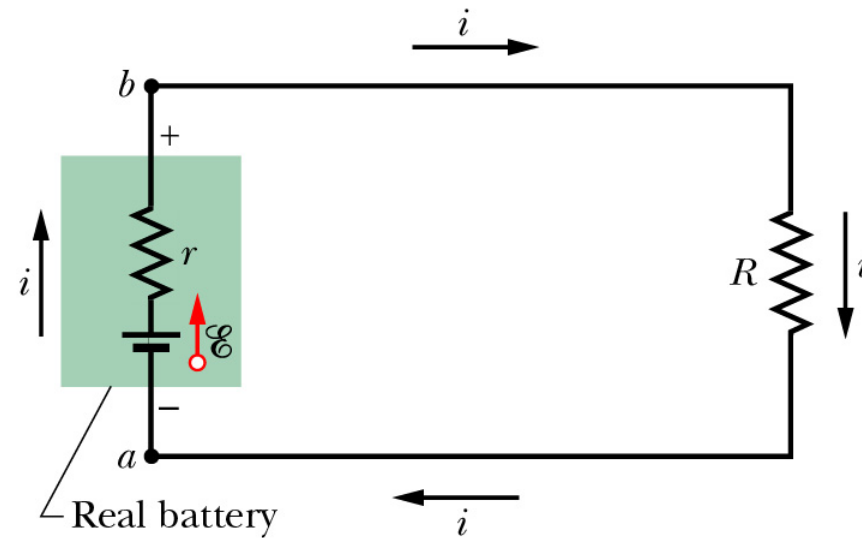Example

- What is the potential difference, V , between points a and b ?
- To find V between any 2 points in circuit
 - Start at one point and traverse circuit to other following any path
 - Add changes in V algebraically



Example

- Moving from b to a clockwise gives


$$V_b - iR = V_a$$

$$V_b - V_a = iR$$

- From loop rule know

$$\mathcal{E} - ir - iR = 0$$


$$i = \frac{\mathcal{E}}{r + R}$$

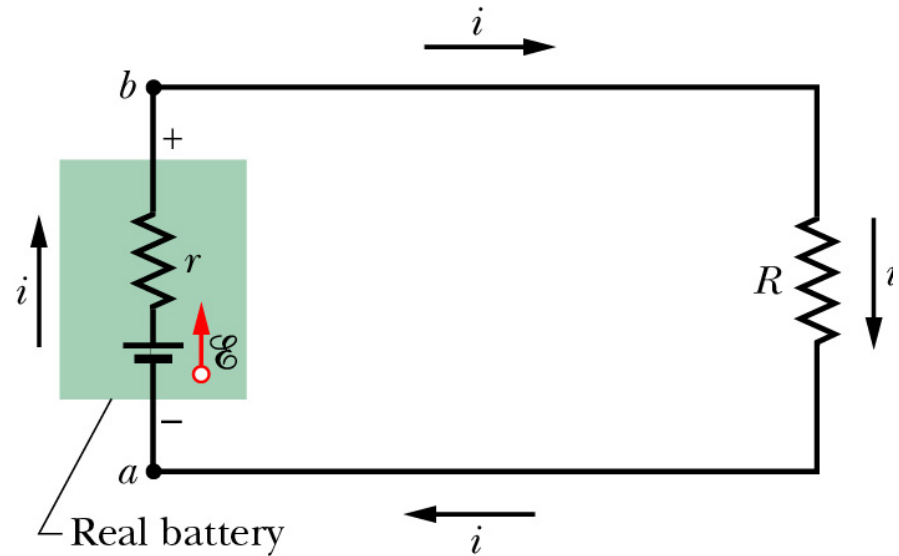

Example

$$V_b - V_a = iR$$

$$i = \frac{\mathcal{E}}{r + R}$$

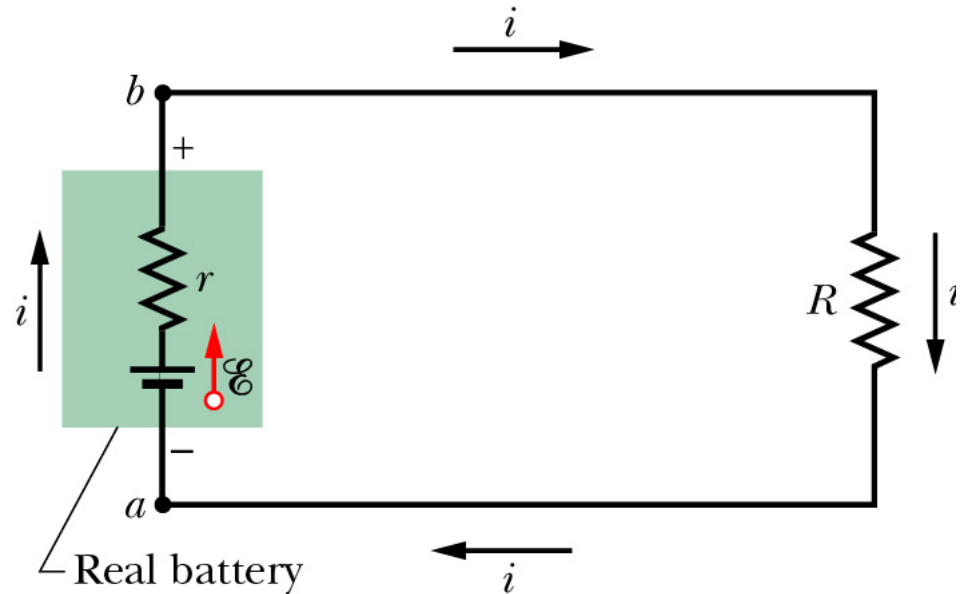

- Substituting for i gives

$$V_b - V_a = \mathcal{E} \frac{R}{R + r}$$

Example

- Now move from b to a counterclockwise


$$V_b + ir - \mathcal{E} = V_a$$

$$V_b - V_a = \mathcal{E} - ir$$

- Substituting i from loop rule


$$i = \frac{\mathcal{E}}{r + R}$$
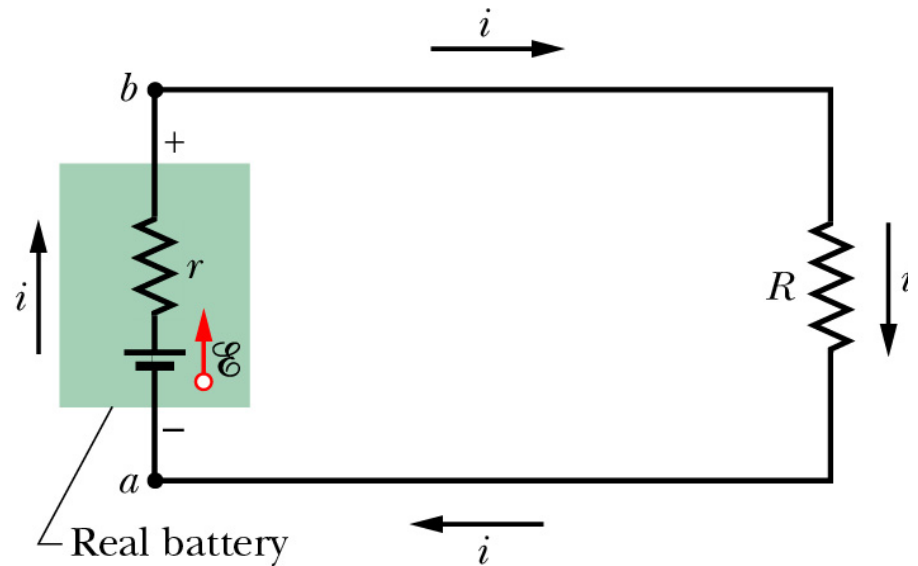
$$V_b - V_a = \mathcal{E} \frac{R}{R + r}$$



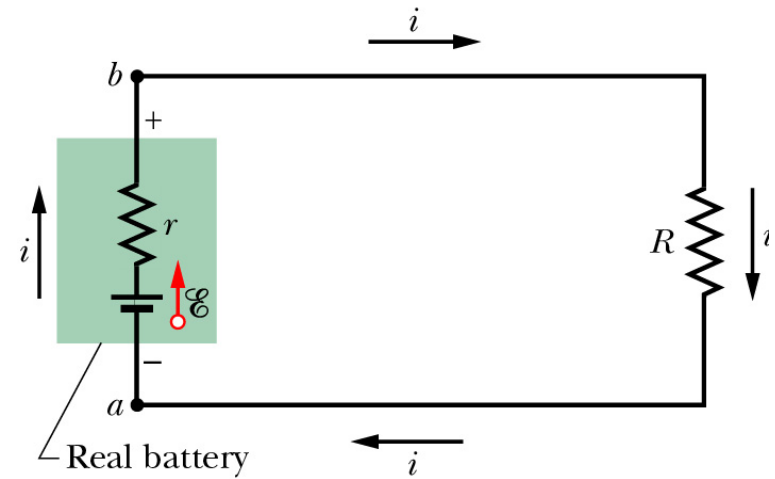Exercise

- Suppose $E = 12V$, $R=10\ \Omega$ and $r=2\ \Omega$
- Potential across battery's terminals is



$$V_b - V_a = E \frac{R}{R + r} = (12V) \frac{10\Omega}{10\Omega + 2\Omega} = 10V$$

- V across terminals only equal to E if no internal resistance ($r=0$) or no current ($i=0$)