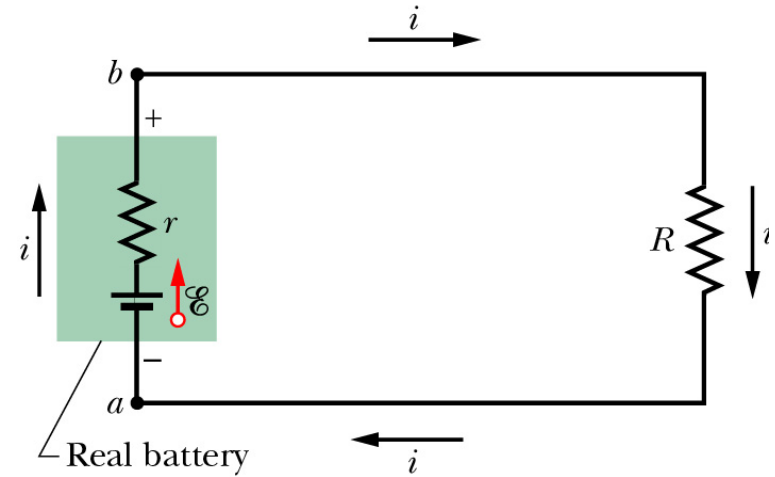


Exercise

- Suppose $E = 12V$, $R=10\ \Omega$ and $r=2\ \Omega$
- Potential across battery's terminals is




$$V_b - V_a = E \frac{R}{R + r} = (12V) \frac{10\Omega}{10\Omega + 2\Omega} = 10V$$

- V across terminals only equal to E if no internal resistance ($r=0$) or no current ($i=0$)

Review

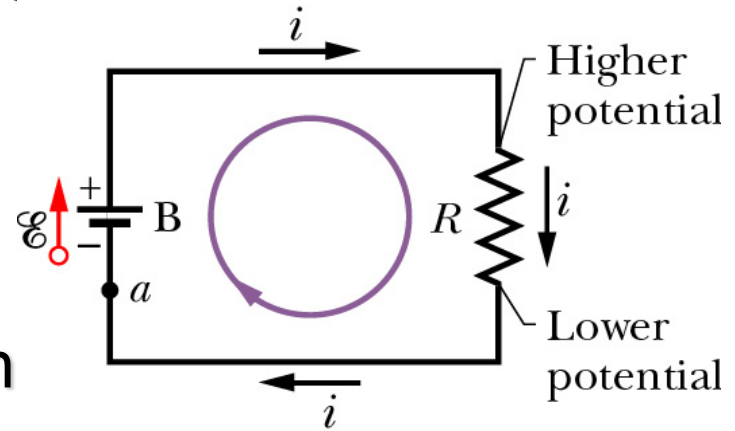- **Kirchhoff's loop rule** – in traversing a circuit loop the sum of the changes in V is zero, $\Delta V = 0$
- **Resistance rule** – Move through resistor in direction of current $V = -iR$ (+ to -; higher to lower), in opposite direction $V = +iR$ (- to +; up the hill).
- **Emf rule** – Move through emf device $V = +E$ going - to +, in opposite direction $V = -E$.




Resistors in Series

- **Resistors in series** (one path from b to a)
- Have identical currents, i , through them
- Use Kirchhoff's loop rule

$$\mathcal{E} - iR_1 - iR_2 - iR_3 = 0$$
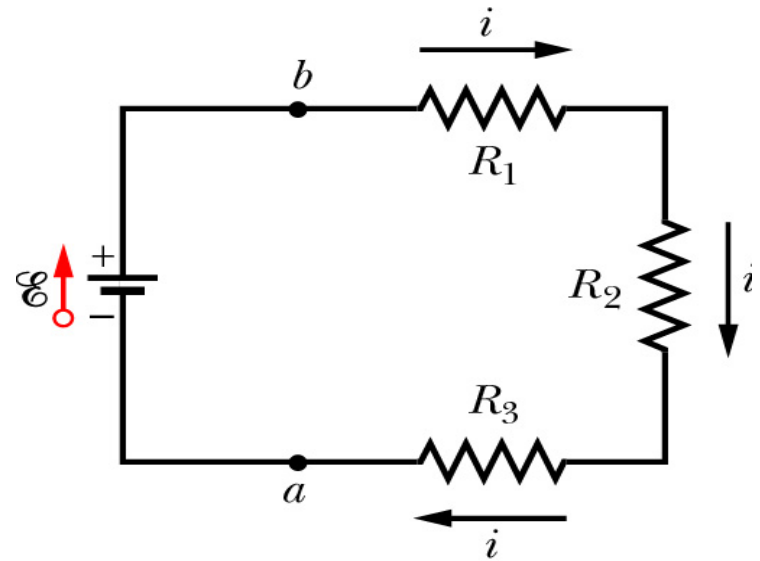
$$i = \frac{\mathcal{E}}{R_1 + R_2 + R_3}$$




Resistors in Series


- Resistors in series
- The 3 resistors act the same as an equivalent resistor R_{eq} .

$$i = \frac{E}{R_1 + R_2 + R_3} = \frac{E}{R_{eq}}$$

$$R_{eq} = R_1 + R_2 + R_3$$

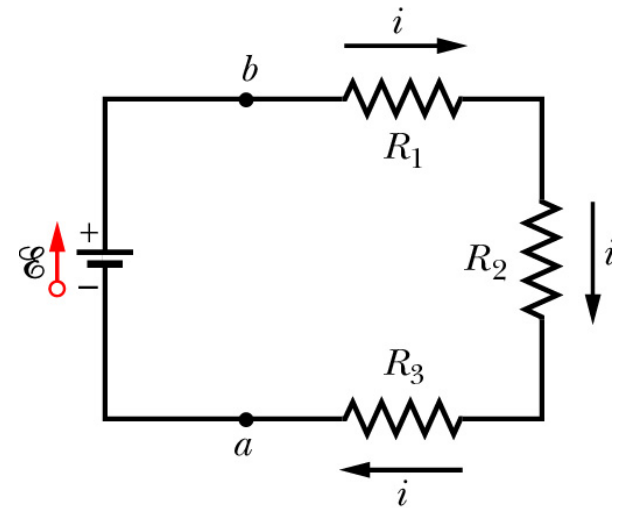

(a)

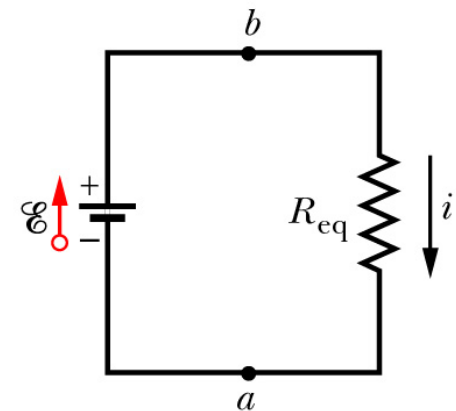


(b)


Resistors in Series

- Resistors in series
- Resistors have identical currents, i
- Sum of V 's across resistors = applied V
- R_{eq} is sum of all resistors

$$R_{eq} = \sum_{j=1}^n R_j$$

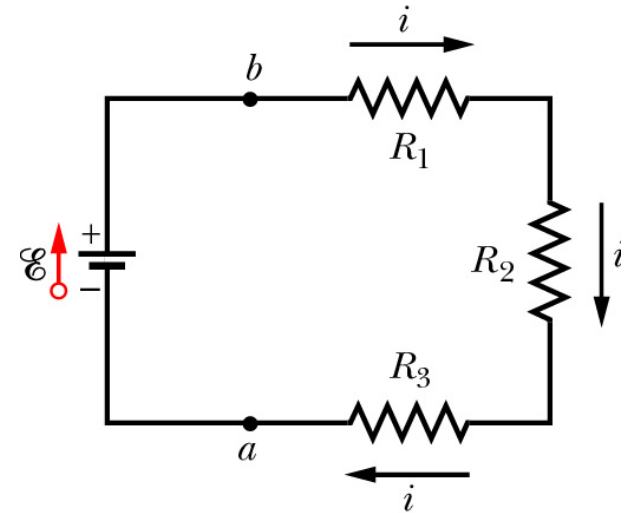

(a)

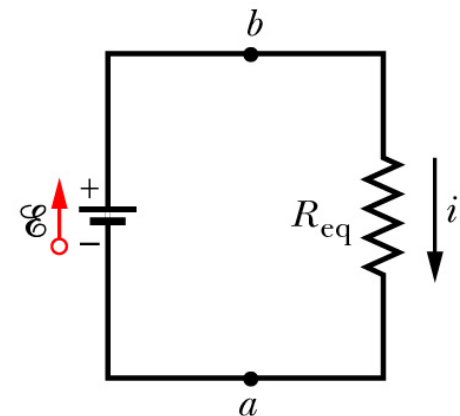


(b)

Exercise

- If $R_1 > R_2 > R_3$, rank greatest first
- A) current through resistors
 i is same for all, tie


$$V = iR$$

- B) V across them
 R_1, R_2, R_3

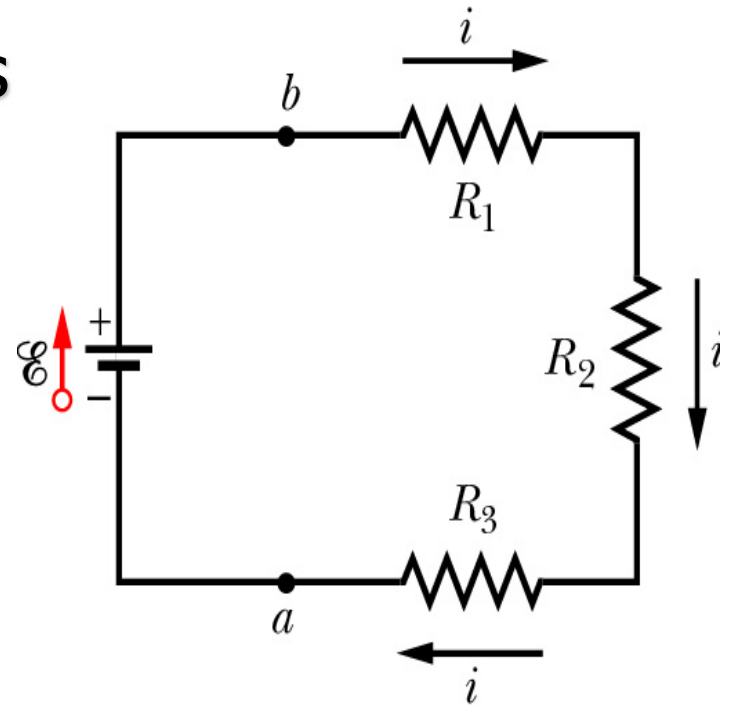

Resistors in Parallel

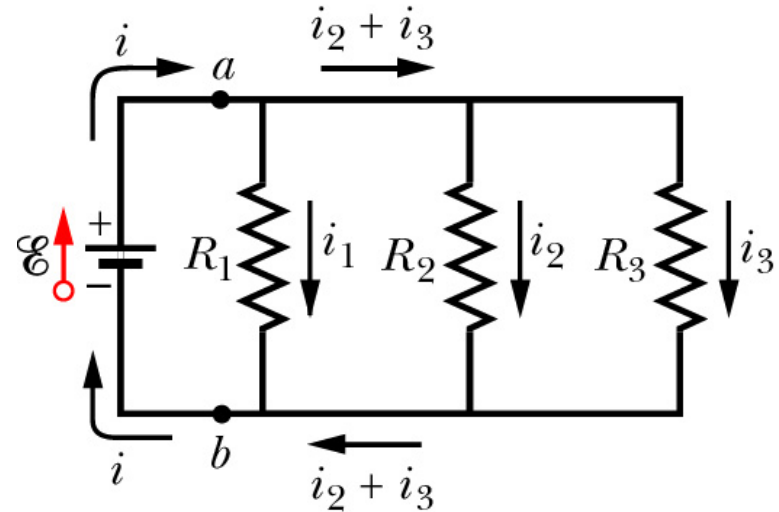- Resistors in parallel
- Have same V across them
- Arbitrarily choose direction for currents in each branch
- Write down current relation for each resistor




$$i_1 = \frac{V}{R_1}$$

$$i_2 = \frac{V}{R_2}$$

$$i_3 = \frac{V}{R_3}$$

Resistors in Parallel

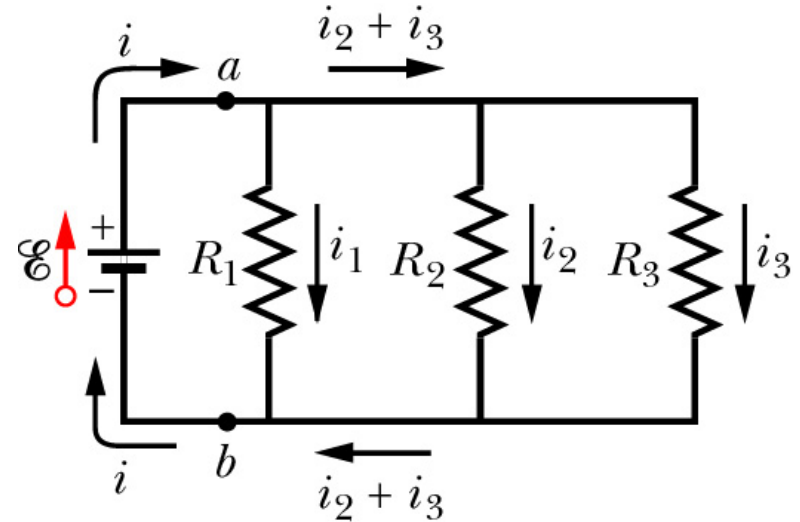- **Resistors in parallel** (more than one path from a to b)
- Apply Kirchhoff's junction rule at point a
- Substitute current values




$$i = i_1 + i_2 + i_3$$


$$i = V \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

Resistors in Parallel

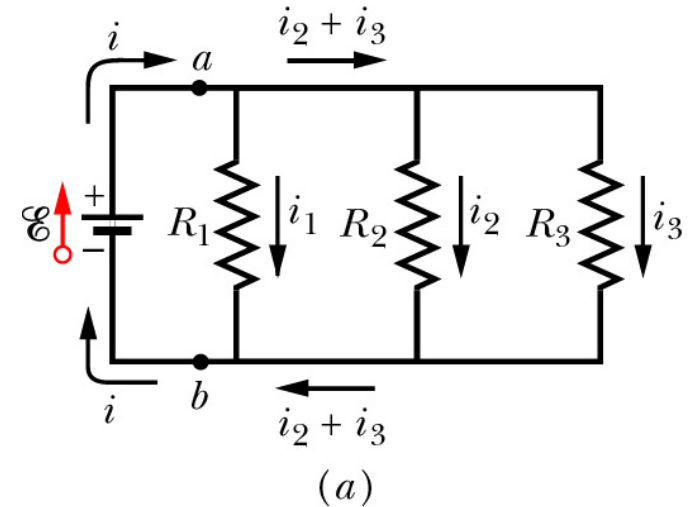- Resistors in parallel
- Replace 3 resistors with equivalent resistor, R_{eq}


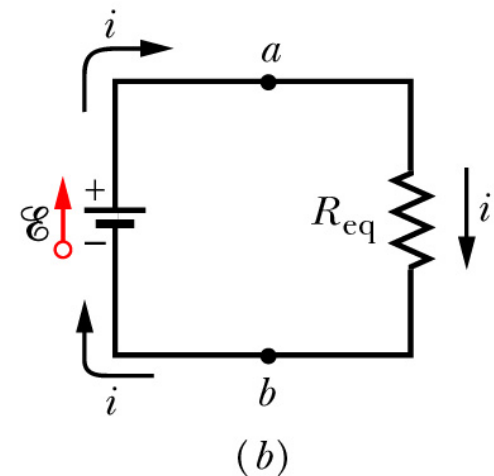
$$\frac{1}{R_{eq}} = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$



Exercise

- Battery with potential V supplies current i to 2 identical resistors
- What is V across and i through either of the resistors if they are connected in
- A) Series – What is constant?

i is same, $V_1 = V/2$

- B) Parallel – What is constant?

V is same, $i_1 = i/2$

$$V = iR$$

Resistors and Capacitors

- Resistors

- Series

$$R_{eq} = \sum_{j=1}^n R_j$$

- Parallel

$$\frac{1}{R_{eq}} = \sum_{j=1}^n \frac{1}{R_j}$$

- Capacitors

- Series

$$\frac{1}{C_{eq}} = \sum_{j=1}^n \frac{1}{C_j}$$

- Parallel

$$C_{eq} = \sum_{j=1}^n C_j$$

How to Analyze Complex Circuits


- **Kirchhoff's junction rule (or current law) –**
 - From conservation of charge
 - Sum of currents entering a junction is equal to sum of currents leaving that junction

- **Kirchhoff's loop rule (or voltage law) –**
 - From conservation of energy
 - Sum of changes in potential going around a complete circuit loop equals zero

Kirchhoff's Rule #1

- Arbitrarily label currents, using different subscript for each branch
- Using conservation of charge at each junction

$$i_{in} = i_{out}$$

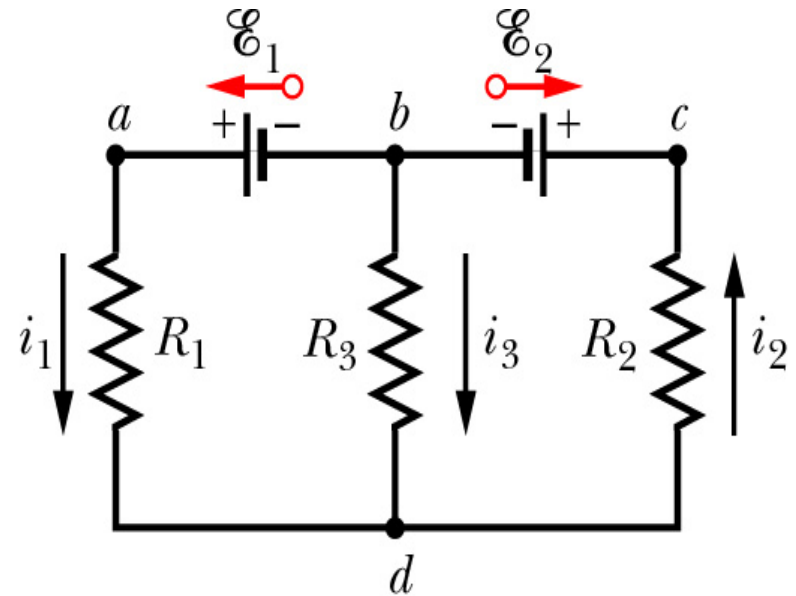

- At point d

$$i_1 + i_3 = i_2$$

- At point b

$$i_1 + i_3 = i_2$$

- At point a



$$i_1 = i_1$$

- At point c

$$i_2 = i_2$$


Exercise

- What is i of the circuit?

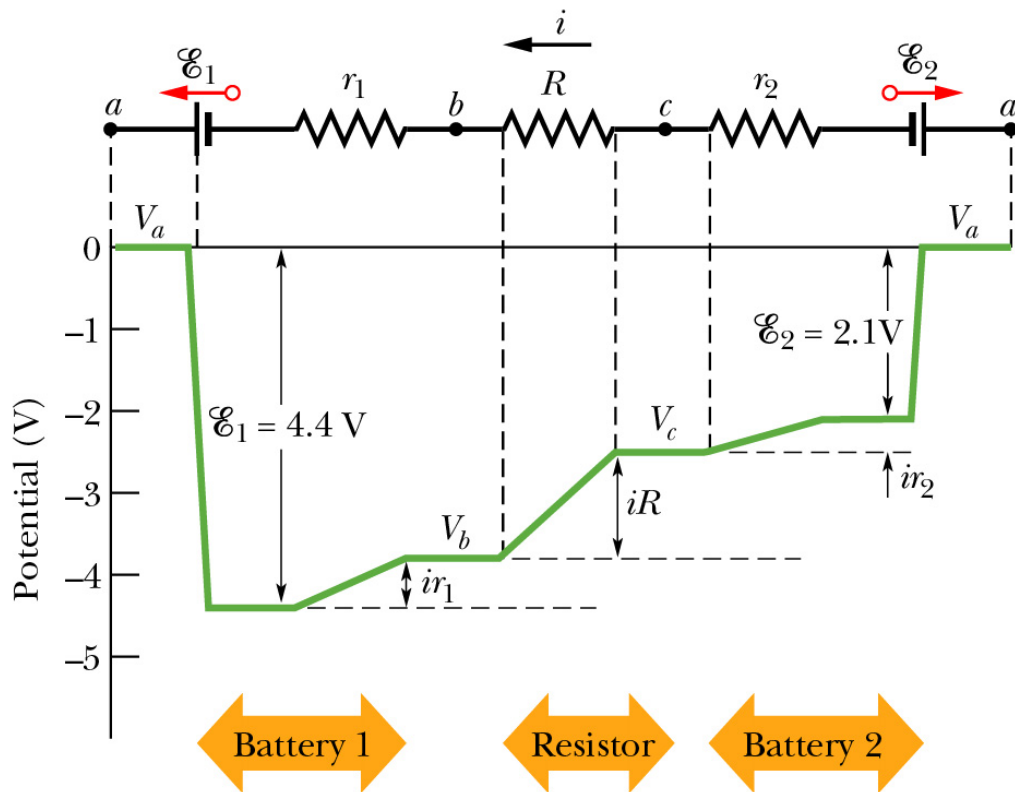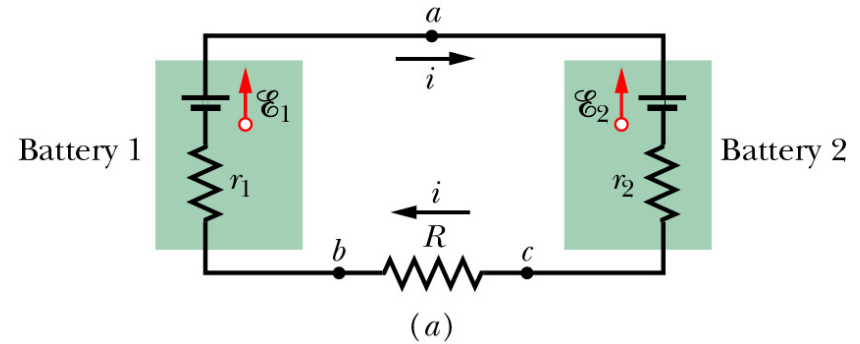

(b)

- Use Kirchhoff's loop rule

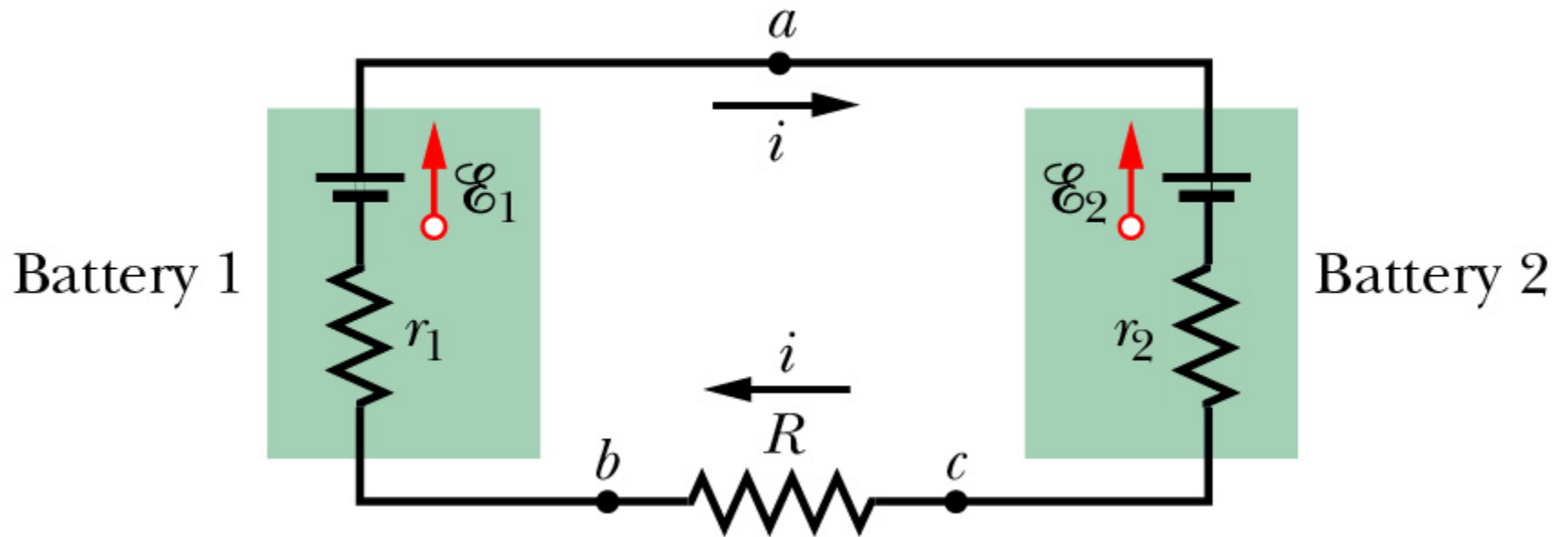

- Clockwise from point a gives

$$-\mathbf{E}_2 - ir_2 - iR - ir_1 + \mathbf{E}_1 = 0$$

- Counterclockwise from point a gives

$$-\mathbf{E}_1 + ir_1 + iR + ir_2 + \mathbf{E}_2 = 0$$

Exercise

• Solve for i
$$-\mathbf{E}_1 + ir_1 + iR + ir_2 + \mathbf{E}_2 = 0$$

$$i = \frac{\mathbf{E}_1 - \mathbf{E}_2}{R + r_1 + r_2}$$

$$\mathbf{E}_1 = 4.4\text{V}$$


$$\mathbf{E}_2 = 2.1\text{V}$$

$$r_1 = 2.3\Omega$$

$$r_2 = 1.8\Omega$$

$$R = 5.5\Omega$$
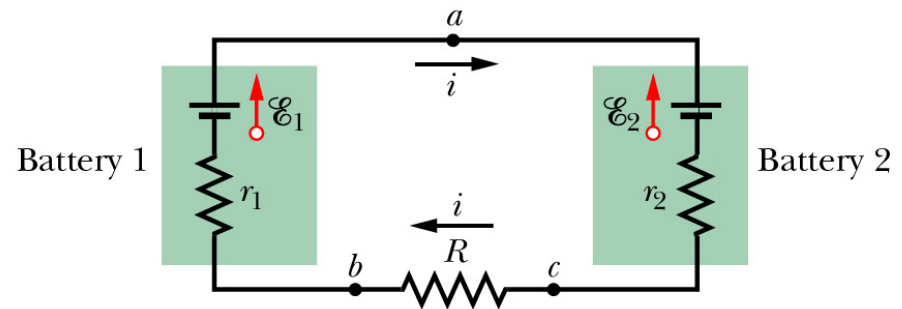
$$i = 0.2396\text{A} \approx 240\text{mA}$$



Exercise

• A real battery has $\mathcal{E} = 12\text{V}$ and $r = 2\Omega$.
Is the V across the terminals greater than, less than or equal to 12V if the current in the battery is

• A) from $-$ to $+$ terminal

LESS THAN

$$V_a + \mathcal{E} - ir = V_b$$

• B) from $+$ to $-$

GREATER THAN

$$V_a + \mathcal{E} + ir = V_b$$

• C) $i = 0$

EQUAL TO 12V

