
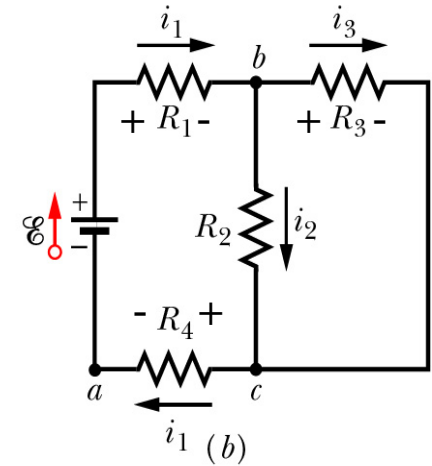


How to Analyze Complex Circuits

- **Kirchhoff's junction rule (or current law) –**
 - From conservation of charge
 - Sum of currents entering a junction is equal to sum of currents leaving that junction
- **Kirchhoff's loop rule (or voltage law) –**
 - From conservation of energy
 - Sum of changes in potential going around a complete circuit loop equals zero

Circuits

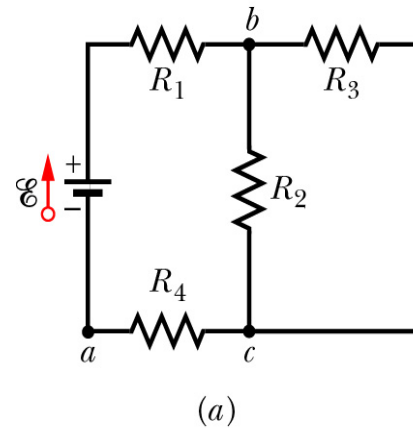- What is i through the battery?
- Label currents. New label for every branch. Pick any arbitrary direction.
- i through R_1 or R_4 is same as for battery
- Can use loop rule




$$\mathcal{E} - i_1 R_1 - i_2 R_2 - i_1 R_4 = 0$$

Circuits

$$\mathcal{E} - i_1 R_1 - i_2 R_2 - i_1 R_4 = 0$$

- Equation has too many unknowns so need to apply loop rule again
- Take the loop through R_2 and R_3

$$-i_3 R_3 + i_2 R_2 = 0$$

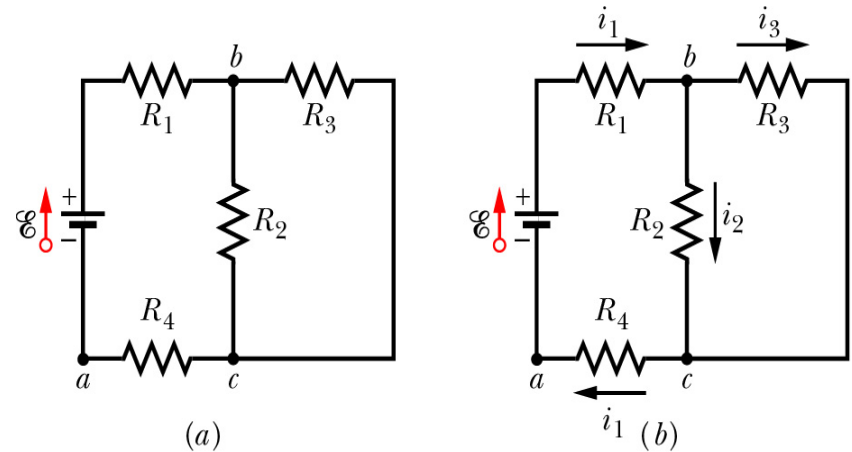

$$i_1 = i_2 + i_3$$

$$-(i_1 - i_2)R_3 + i_2 R_2 = 0$$

$$i_2 = -\frac{i_1 R_3}{(R_3 + R_2)}$$


Circuits

Now solve for i_1 :


$$E - i_1 R_1 - i_2 R_2 - i_1 R_4 = 0$$

$$E - i_1 R_1 - \frac{i_1 R_3 R_2}{(R_2 + R_3)} - i_1 R_4 = 0$$
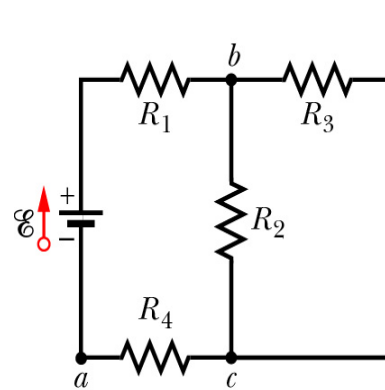
$$i_1 = \frac{E}{R_1 + \frac{R_2 R_3}{(R_2 + R_3)} + R_4}$$



(a)

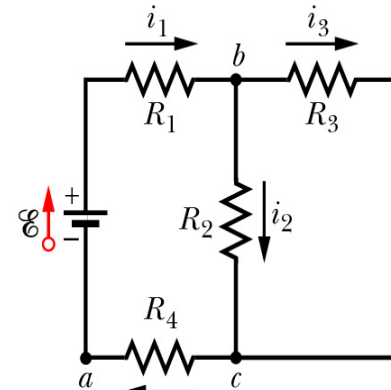


(b)

Circuits

- What is current Voltage lost (V) in R_2 ?
- Recall that $V=iR$

$$V_2 = i_2 R_2$$

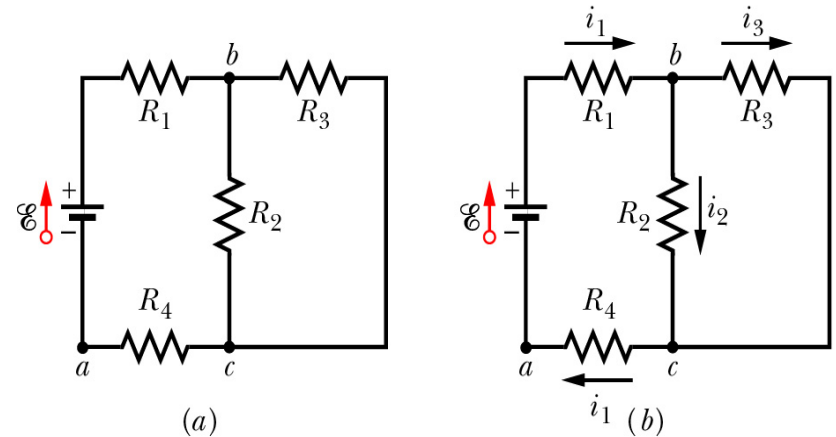


$$E - i_1 R_1 - i_2 R_2 - i_1 R_4 = 0$$

$$i_2 = \frac{i_1 R_1 + i_1 R_4 - E}{R_2}$$

$$i_1 = \frac{E}{R_1 + \frac{R_2 R_3}{(R_2 + R_3)} + R_4}$$


RC - circuit

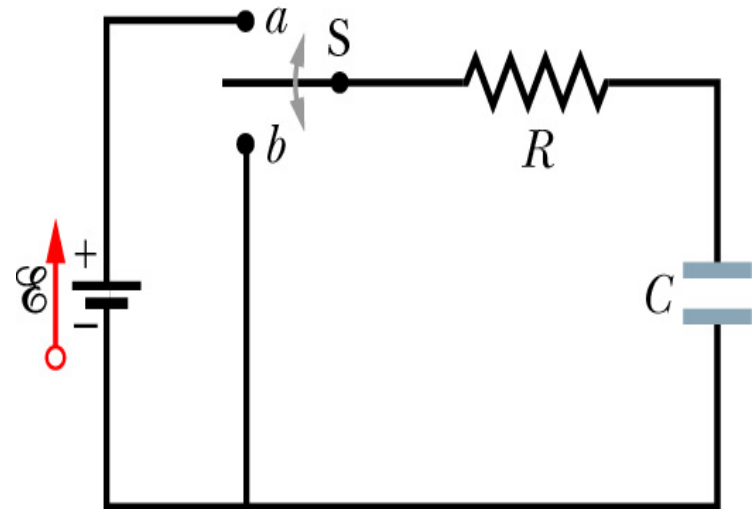- Circuits where current varies with time
- **RC series circuit** – a resistor and capacitor are in series with a battery and a switch
- At $t = 0$ switch is open and capacitor is uncharged so $q = 0$



RC - circuit

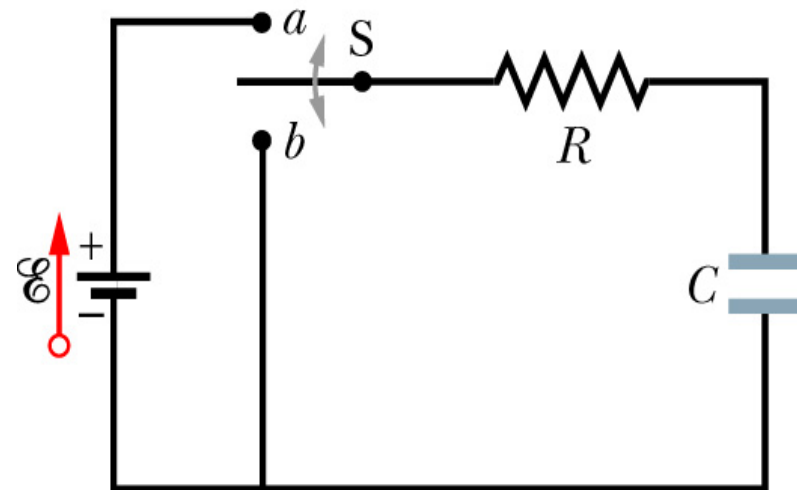- Close the switch at point a
- Charge flows (current) from battery to capacitor, increasing q on plates and V across plates




- When V_C equal $V_{battery}$ flow of charge stops (current is zero) and charge on capacitor is

$$q = CV = CE$$

RC - circuit

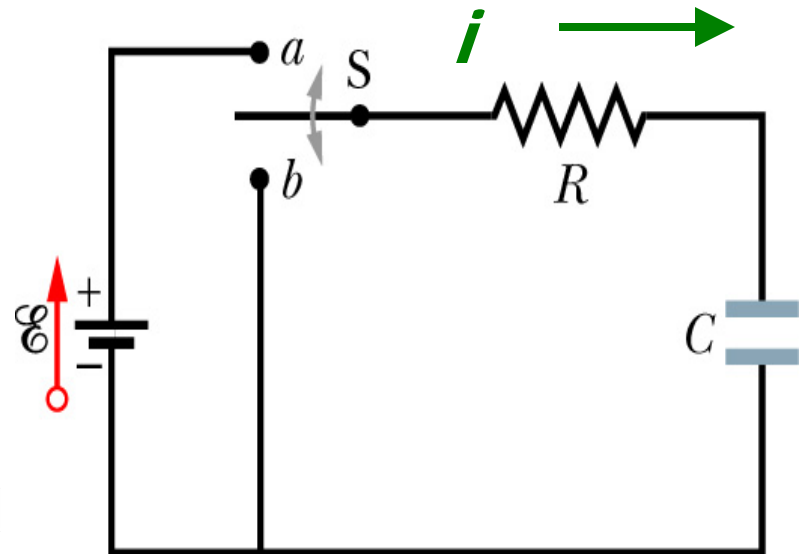- Want to know how q and V of capacitor and i of the circuit change with time when charging the capacitor
- Apply loop rule, traversing clockwise from battery




$$\mathcal{E} - iR - \frac{q}{C} = 0$$

RC - circuit

$$E - iR - \frac{q}{C} = 0$$

- Contains 2 of the variables we want i and q
- Remember

$$i = \frac{dq}{dt}$$

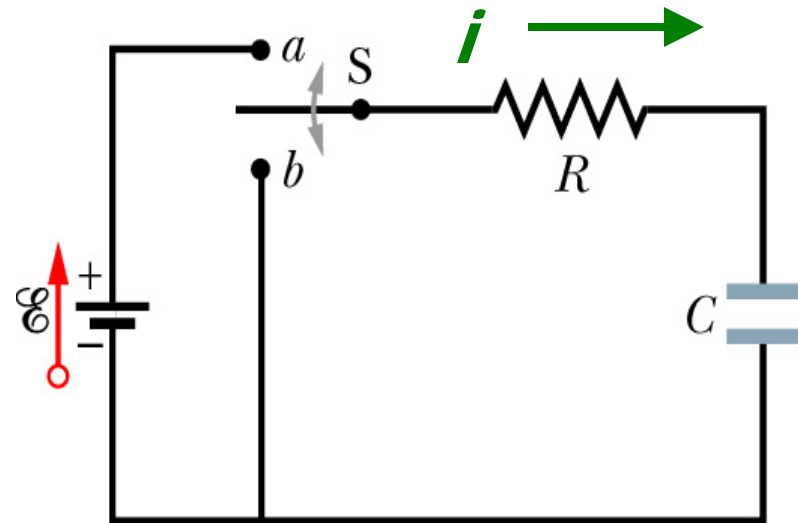


- Substituting gives

$$R \frac{dq}{dt} + \frac{q}{C} = E$$

RC - circuit

$$R \frac{dq}{dt} + \frac{q}{C} = E$$

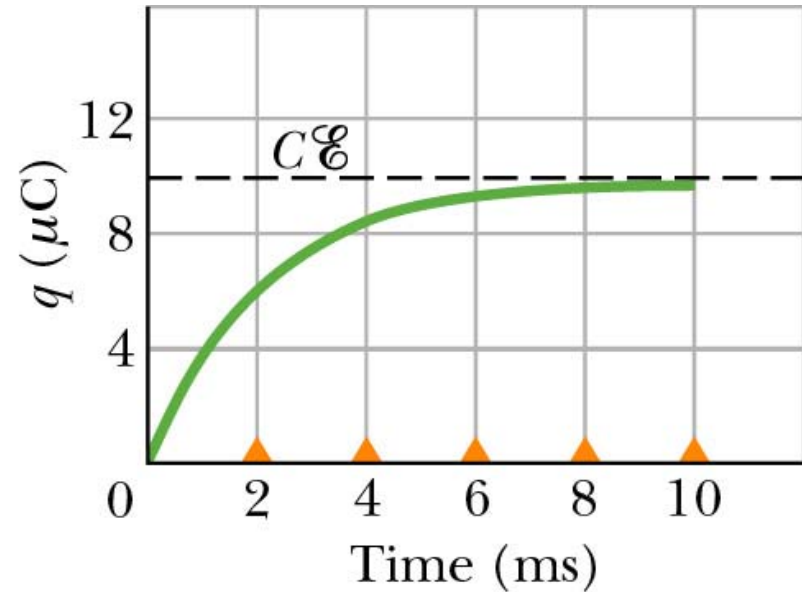- Need a function which satisfies initial condition $q = 0$ at $t = 0$ and final condition of $q = CE$ at $t = \infty$
- For **charging a capacitor**




$$q = CE \left(1 - e^{-t/RC} \right)$$

RC - circuit

$$q = CE \left(1 - e^{-t/RC} \right)$$

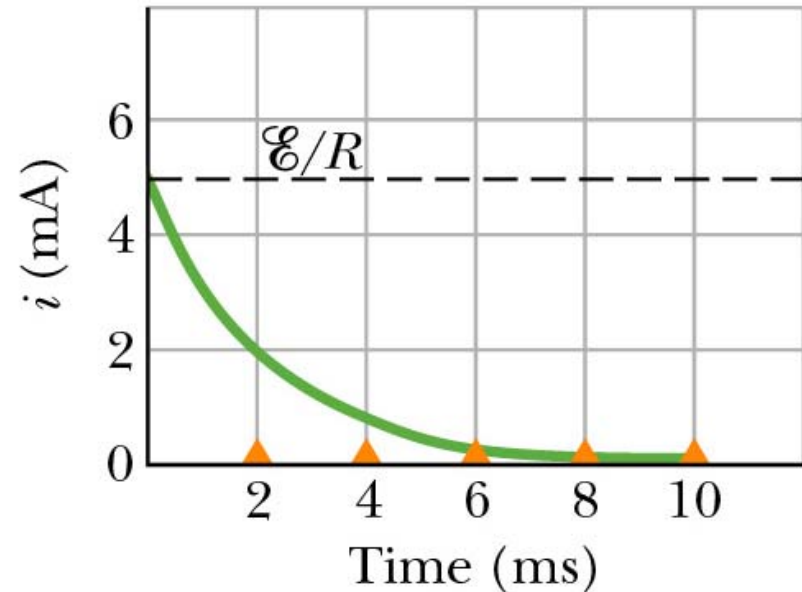- Want current as a function of time
- For **charging a capacitor**




$$i = \frac{dq}{dt} = \left(\frac{E}{R} \right) e^{-t/RC}$$

RC - circuit

$$q = CE \left(1 - e^{-t/RC} \right)$$

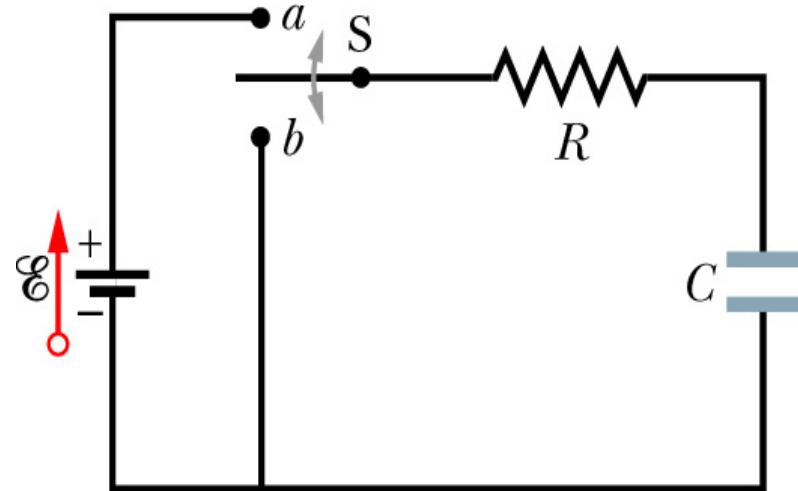
- Want V across the capacitor as function of time
- For **charging a capacitor**



$$V_c = \frac{q}{C} = E \left(1 - e^{-t/RC} \right)$$

RC - circuit

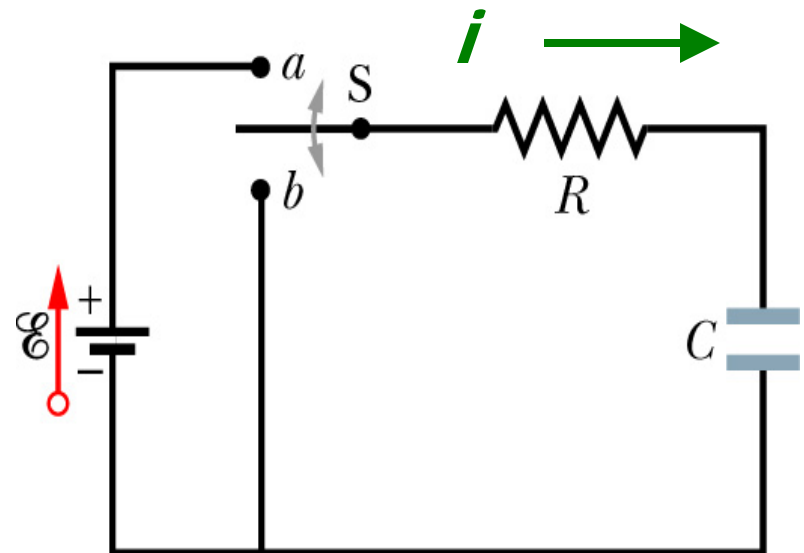- Want to know how q of capacitor and i of the circuit change with time when **discharging** the capacitor
- At new time $t = 0$, throw switch to point b and discharge capacitor through resistor R




RC - circuit

- Apply the loop rule again but this time no battery

$$-iR - \frac{q}{C} = 0$$

- Substituting for i again gives differential equation

$$R \frac{dq}{dt} + \frac{q}{C} = 0$$

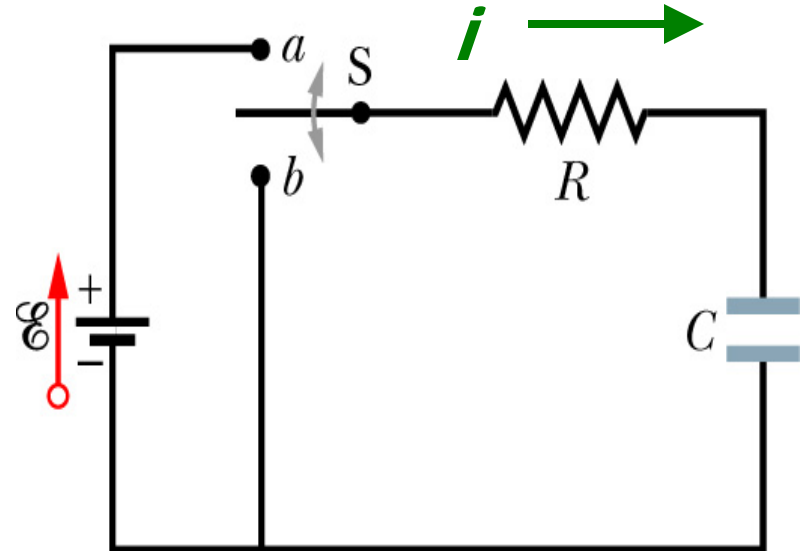


RC - circuit

$$R \frac{dq}{dt} + \frac{q}{C} = 0$$

- Solution must satisfy initial condition that $q_0 = CV_0$
- For **discharging a capacitor**


$$q = q_0 e^{-t/RC}$$

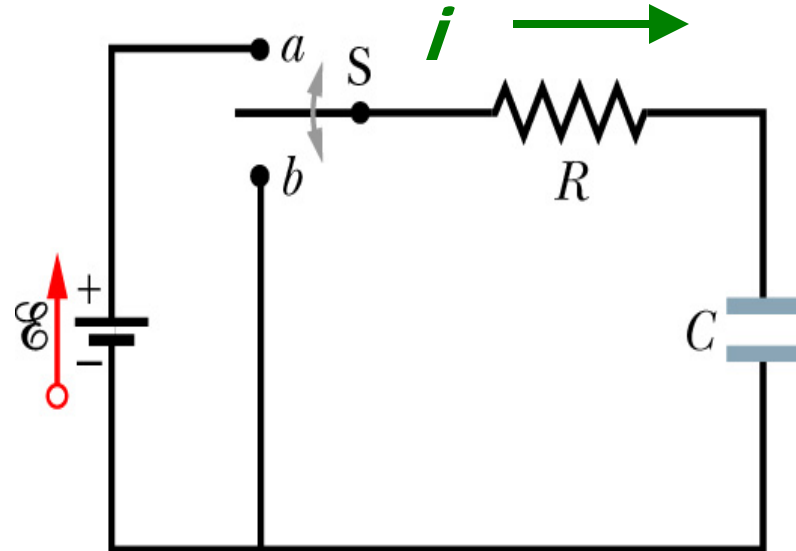

RC - circuit

$$q = q_0 e^{-t/RC}$$

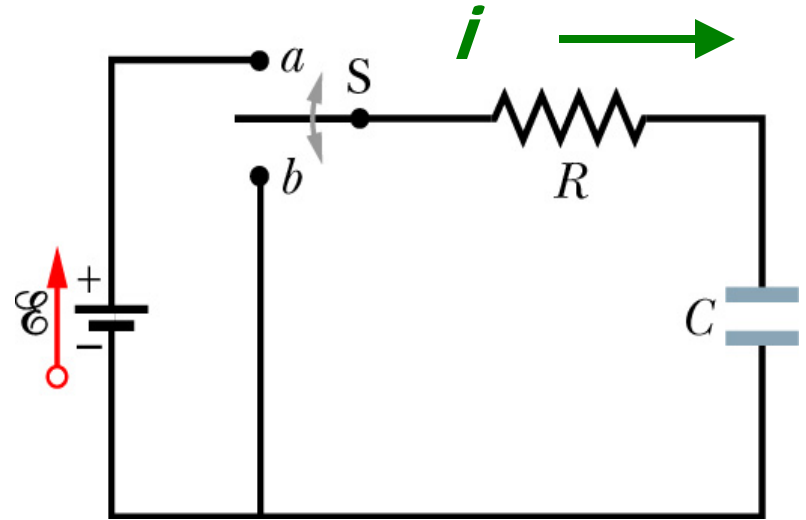- Find i for **discharging capacitor** with initial condition at $i_0 = V_0/R = q_0/RC$ at $t = 0$



$$i = \frac{dq}{dt} = -\left(\frac{q_0}{RC}\right)e^{-t/RC}$$

Negative sign means charge is decreasing

Circuits

- Charging capacitor

$$q = CE(1 - e^{-t/RC})$$

$$i = \left(\frac{E}{R} \right) e^{-t/RC}$$

- Discharging capacitor

$$q = q_0 e^{-t/RC}$$

$$i = - \left(\frac{q_0}{RC} \right) e^{-t/RC}$$

- Define **capacitive time constant** –
greater τ , greater (dis)charging time

$$\tau = RC$$